

ESC201: Lecture 17




Dr. Imon Mondal

ASSISTANT PROFESSOR,
ELECTRICAL ENGINEERING, IIT KANPUR


Digital Circuits

Combinational Circuits

 


Output is determined by current values of inputs only.


Sequential Circuits

 

 Output is determined in general by current values of inputs and past values of inputs/outputs as well.




Memory with Set/Reset Knob

 

Two memory states are possible:


1. $Q1=Q3=0$ (Low), $Q2=1$ (High)
2. $Q1=Q3=1$ (High), $Q2=0$ (Low)

But how will one change the state?

 


We need at least 2 i/p logic gates

 - NOR gate behave like INV if one i/p is 0
- NAND behaves like INV if one i/p is 1




NOR-based SR Latch

 

NAND-based SR Latch

Set-Reset (SR) Latch: Set State

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Re set State

$$\overline{1 + Q} = 0$$

S	R	Q	\bar{Q}	State
1	0	1	0	SET

Set-Reset (SR) Latch: Reset State

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Re set State


$$\overline{1 + \bar{Q}} = 0$$

S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

SR Latch: 'Hold' (memory)

 


S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	0	1	0	HOLD


 


S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	0	1	0	HOLD
0	1	0	1	RESET
0	0	0	1	HOLD

SR Latch: Invalid Input and Gate Delays



 


Suppose gate-1 is faster

  


Q = 1

   On the other hand suppose that gate-2 is faster.




Again the output is unpredictable in general

NOR-based vs NAND-based SR Latch


 


S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\bar{Q}	HOLD
1	1	0	0	INVALID

 


\bar{S}	\bar{R}	Q	\bar{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\bar{Q}	HOLD
0	0	1	1	INVALID

NAND-based SR Latch with Enable

  


Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid

D latch


 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid


 


If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Synchronous Sequential Circuits

  


Example

  


Example

  



Problem with Latch

 

 Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop

  


Positive edge triggered flipflop

  Negative Edge Triggered Latch or Flip-flop



Master-Slave D Flip-flop

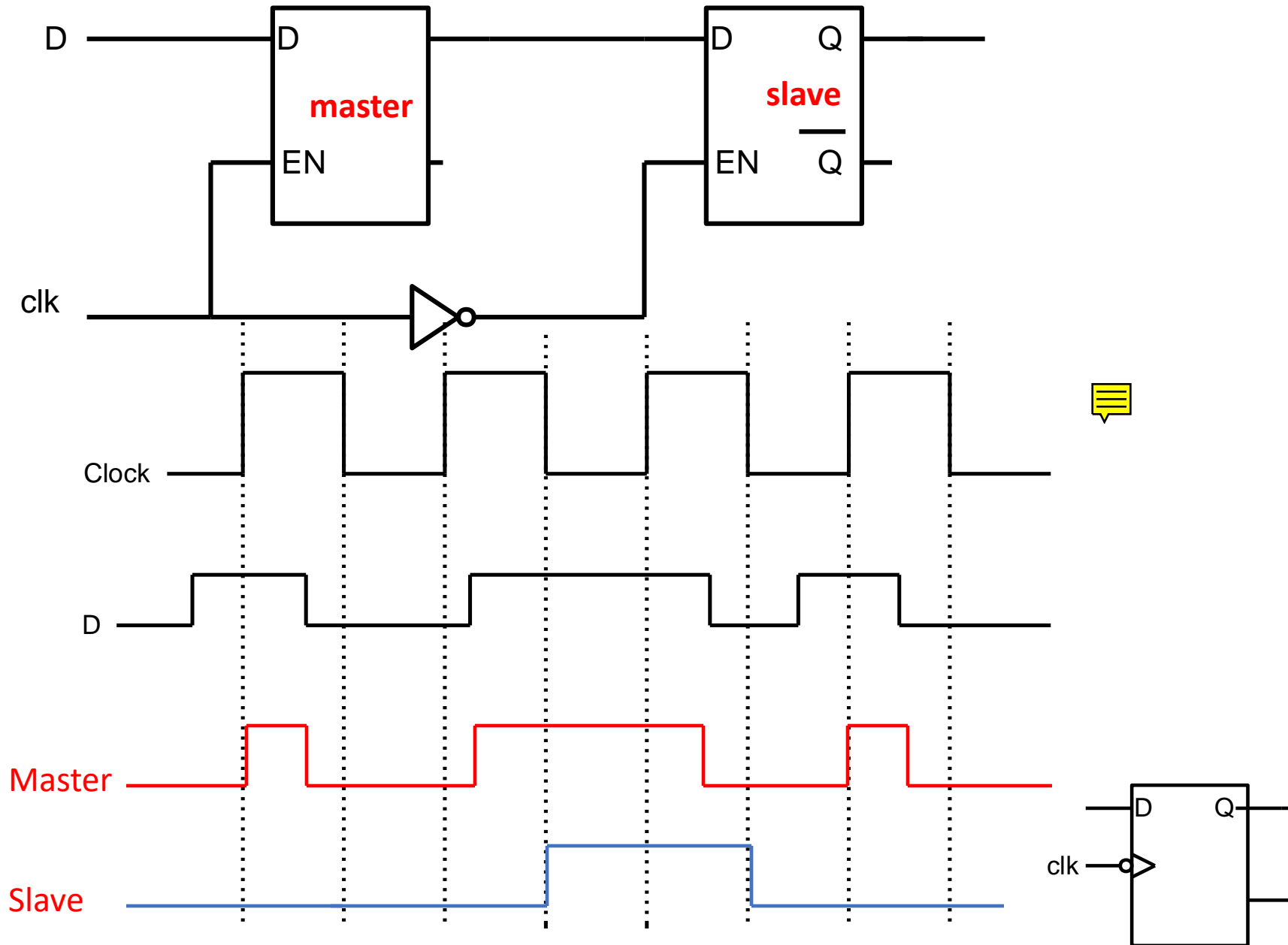


Characteristic Table vs Excitation Table

- What inputs are required for a particular state change?

Excitation table:

		Inputs
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

 


Characteristic table:

Inputs (T)	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table: Examples

 


J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Excitation table: Inputs

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

D	Q(t+1)
0	0
1	1

Excitation table:


Inputs

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Implementing a T Flip Flop using D Flip Flop

 - Suppose D flip flop is given, how do we design a T flip-flop?



T	Q(t)	Q(t+1)	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


Truth table of what we desire to make

At current instant, we have T and Q
How do we get D from signals we have

Q\T	0	1
0		1
1	1	


$$D = \bar{T} \cdot Q(t) + T \bar{Q}(t)$$

$$D = T \oplus Q(t)$$

 

Excitation table of what we have

D Flip Flop to JK Flip Flop

 

J	K	Q(t+1)	D
0	0	Q(t)	Q(t)
0	1	0	0
1	0	1	1
1	1	$\overline{Q(t)}$	$\overline{Q(t)}$

Truth table of what we desire to make

Expanded Form

J	K	Q	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


Excitation table of what we have

D
0
1
0
0
1
1
1
0


At current instant, we have J,K and Q
D from signals we have

JK \ Q	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = \overline{Q}.J + Q.\overline{K}$$


 


D Latch: MUX based Implementation

 


EN	D	Q	Description
0	X	Q	Hold
1	1	1	Set
1	0	0	Reset

Transparent when EN is high

  


Sequential Circuits

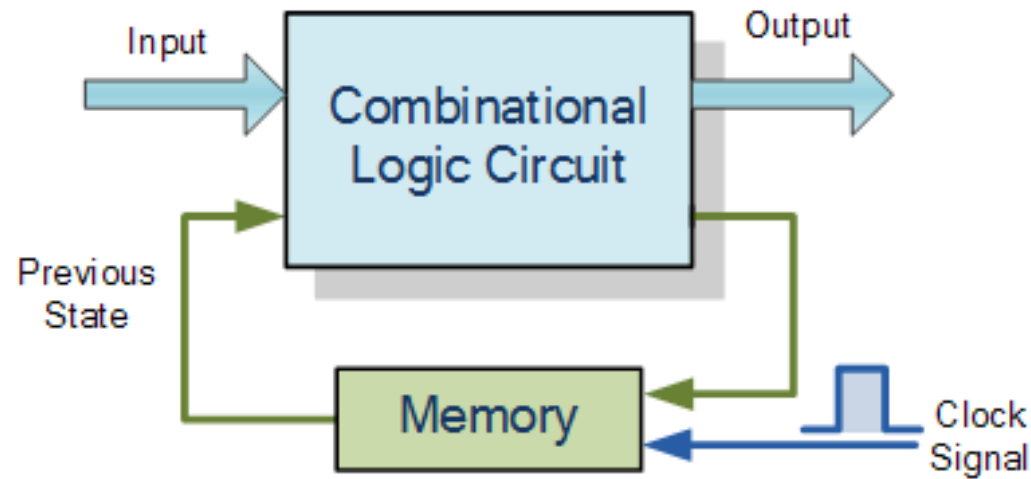


- Calculation divided into steps
- Each step is triggered by a clock
- At each step,
 - output is based on the current values of inputs and past values of inputs/outputs.
- Requires memory

D Flip Flop as 1 bit Storage/Memory

 


Inputs (D)	Q(t+1)
0	0
1	1

$$Q(t + 1) = D$$

 

Synchronous Clocked Sequential Circuits

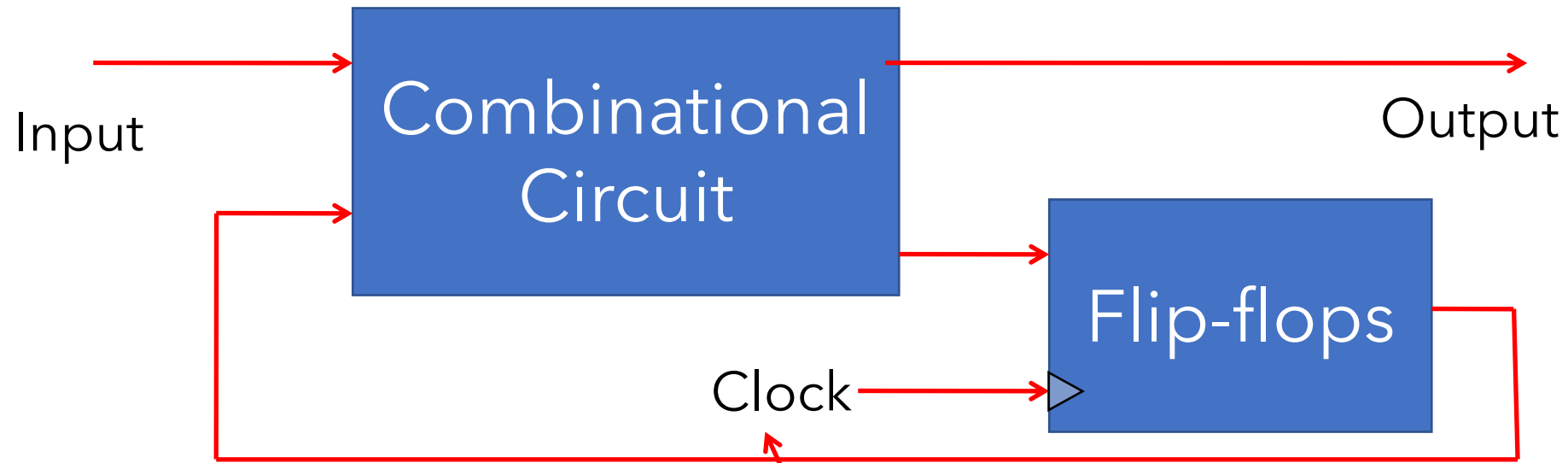


Entire operation synchronized via clock


Employs signals that affect the stored value only at discrete instants of time.

Synchronization is achieved via the **clock pulses**.

Sequential Circuit “unrolled” in Time

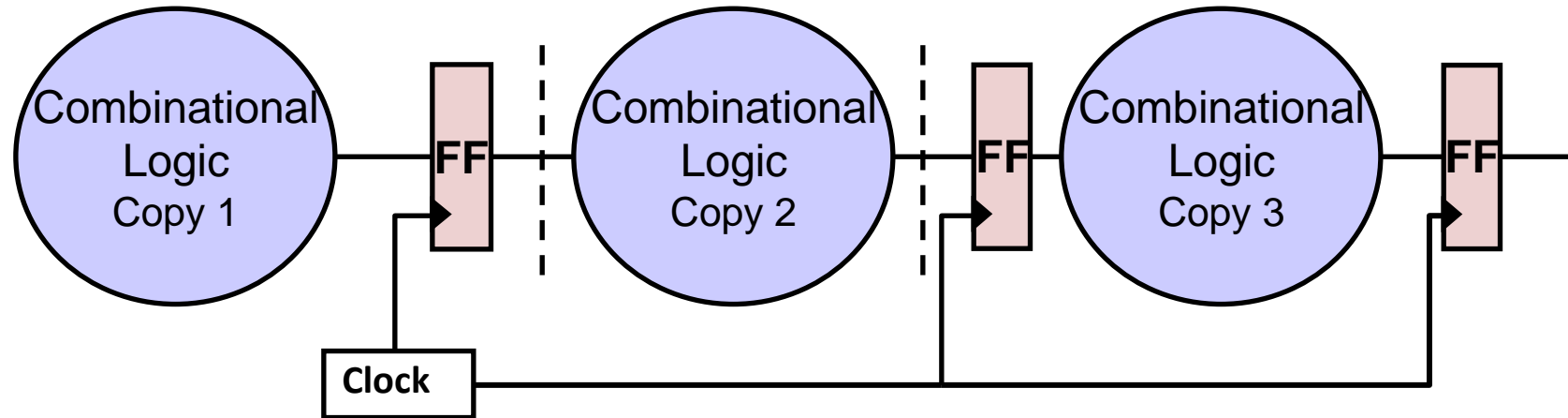

Sequential Circuits

 


The binary information stored in the storage elements at any given time defines the **state** of the sequential circuit at that time

Output is a function of input as well as the present state (the stored value).

Next state is also a function of the present state and inputs.

Analyzing sequential circuits

 

- Output z depends on the input x and on the state of the memory (A, B)
- The memory has 2 FFs and each FF can be in state 0 or 1.
- Thus there are four possible states: AB : 00,01,10,11
- To describe the behavior of a sequential circuit, we need to show
 - How the system goes from one memory state to the next as the input changes
 - How the output responds to input in each state