

ESC201: Lecture 12




Dr. Imon Mondal

ASSISTANT PROFESSOR,
ELECTRICAL ENGINEERING, IIT KANPUR

Digital Processing and Other Gates

 - Recall that we only have two values: 0 & 1
 - Map naturally to logic TRUE (T) and FALSE (F)
 - Can also represent numbers
- We need to realize all functions using 0 and 1
- Boolean logic (X, Y, Z are digital signals "0" and "1")
 - If X is true and Y is true then Z is true else Z is false
 - $Z = X \text{ AND } Y$ or $Z = X \cdot Y$



AND gate

Truth table

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


Enumeration of all possible input combinations

AND & OR Gates

AND of two logic values

$$\text{AND: } y = x_1 \cdot x_2$$


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 

OR of two logic values


$$\text{OR: } y = x_1 + x_2$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

 


Logic Gates


AND: $y = x_1 \cdot x_2$

 

OR: $y = x_1 + x_2$

 


NOT: $y = \bar{x}$

 


AND Gate?

- AND of two logic values

$$\text{AND: } y = x_1 \cdot x_2$$

 

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 


➤ No, the gain is always less than 1 \Rightarrow no noise immunity


OR Gate?

- OR of two logic values

$$\text{OR: } y = x_1 + x_2$$

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

 


➤ No, the gain is always less than 1 \Rightarrow no noise immunity


Elementary Logic Gates

Elementary Gates


AND: $y = x_1 \cdot x_2$

 

OR: $y = x_1 + x_2$

 


NOT: $y = \bar{x}$

 


NAND & NOR Gates



NAND: $y = \overline{x_1 \cdot x_2}$

 

NOR: $y = \overline{x_1 + x_2}$

 


NAND & NOR Gates: Universal Gates

  

c_1	c_2	V_o
0	0	1
0	1	1
1	0	1
1	1	0

NAND gate

 


c_1	c_2	V_o
0	0	1
0	1	0
1	0	0
1	1	0



NOR gate

□ NAND and NOR are universal gates.


NAND & NOR Gates: NMOS Implementation

 

NAND gate

  

NOR gate

 


□ NAND and NOR are universal gates.

Logic Gates


$$\text{NAND: } y = \overline{x_1 \cdot x_2}$$


 
$$\text{NOR: } y = \overline{x_1 + x_2}$$



 
$$\text{XOR: } y = x_1 \oplus x_2 = x_1 \cdot \overline{x_2} + \overline{x_1} \cdot x_2$$




A typical intel core i7 processor has about 500 million (5×10^8) logic gates

Gates with more than 2 inputs


AND: $y = x_1 \cdot x_2 \cdot x_3 \dots$

 


OR: $y = x_1 + x_2 + x_3 + \dots$

 

 Multiple-input NAND & NOR Gates Implementation



n-input NAND gate

 

n-input NOR gate

Boolean Operators

- Basic operators

$$\text{AND: } y = x_1 \cdot x_2$$

$$\text{OR: } y = x_1 + x_2$$

$$\text{NOT: } y = \bar{x}$$

x_1	x_2	y
0	0	0
0	1	0
1	0	0
1	1	1

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	1

x	y
0	1
1	0

Truth Tables shows all possible values of an output for all possible combinations of inputs

How to show equivalency of two expressions?

- Compare the truth table on both side
- Show $x + x = x$

x	x	$x + x$
0	0	0
1	1	1

How to show equivalency of two expressions?

- Compare the truth table on both side
- Show $\overline{x \cdot y} = (\bar{x} + \bar{y})$

x	y	$\overline{x \cdot y}$	$(\bar{x} + \bar{y})$
0	0	1	1
1	0	1	1
0	1	1	1
1	1	0	0

Basic Postulates and Theorems

- Every algebra has basic theorems/postulates regarding operators
- OR & AND are not exactly like Addition & Multiplication operators
- Commutative

$$x + y = y + x$$

$$x \cdot y = y \cdot x$$

- Distributive

$$x \cdot (y + z) = x \cdot y + x \cdot z$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

Basic Postulates and Theorems

P1.a: $x + 0 = x$

P1.b: $x \cdot 1 = x$

Identity element

P2.a: $x + y = y + x$

P2.b: $x \cdot y = y \cdot x$

Commutative

P3.a: $x \cdot (y + z) = x \cdot y + x \cdot z$

P3.b: $x + y \cdot z = (x + y) \cdot (x + z)$

Distributive

P4.a: $x + \bar{x} = 1$

P4.b: $x \cdot \bar{x} = 0$

Complement

T1.a: $x + x = x$

T1.b: $x \cdot x = x$

T2.a: $x + 1 = 1$

T2.b: $x \cdot 0 = 0$

T3.a: $\overline{(\bar{x})} = x$

T4.b: $x \cdot (y \cdot z) = (x \cdot y) \cdot z$

T4.a: $x + (y + z) = (x + y) + z$

T5.a: $\overline{(x + y)} = \bar{x} \cdot \bar{y}$

T5.b: $\overline{(x \cdot y)} = \bar{x} + \bar{y}$

DeMorgan's Theorem

T6.a: $x + x \cdot y = x$

T6.b: $x \cdot (x + y) = x$

How to verify an expression?

- Using truth tables
- Showing using postulates

$$\overline{(\overline{x_1 \cdot x_2} + \overline{x_2 \cdot x_3})} = x_1 \cdot x_2 + \overline{x_2} \cdot x_2 + x_1 \cdot \overline{x_3} + \overline{x_2} \cdot \overline{x_3}$$

Boolean Algebra

$$\overline{(\overline{x_1} \cdot x_2 + \overline{x_2} \cdot x_3)} = (\overline{\overline{x_1} \cdot x_2}) \cdot (\overline{\overline{x_2} \cdot x_3})$$

$$= (\overline{\overline{x_1}} + \overline{x_2}) \cdot (\overline{\overline{x_2}} + \overline{x_3})$$

$$= (x_1 + \overline{x_2}) \cdot (x_2 + \overline{x_3})$$

$$= x_1 \cdot x_2 + \overline{x_2} \cdot x_2 + x_1 \cdot \overline{x_3} + \overline{x_2} \cdot \overline{x_3}$$


$$= x_1 \cdot x_2 + x_1 \cdot \overline{x_3} + \overline{x_2} \cdot \overline{x_3}$$

Calculation using Binary System

- Binary signals represent logic states
 - can implement any logic
 - logic consists of AND, OR & NOT condition
 - Boolean Algebra
- Binary signals can represent any numbers
 - We can do all arithmetic over it
 - Enables any calculations
 - Addition, Subtraction, Multiplication, Division, etc.
- Computers can do calculations
 - evaluate logic states and make decision over that

How to do such
calculations?

Addition

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table


$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

How to get this expression?

How to get this gate implementation?

 

 How to get an expression from truth table?



x_1	x_2	y
0	0	0
0	1	1
1	0	0
1	1	0

$y = 1$ when x_1 is 0 and x_2 is 1

Boolean expression

$$y = \overline{x_1} \cdot x_2$$

(NOT x_1) AND x_2

How to get an expression from truth table?

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	0

$y = \overline{x_1} \cdot \overline{x_2}$

x_1	x_2	y
0	0	0
0	1	0
1	0	1
1	1	0

$y = x_1 \cdot \overline{x_2}$

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$

$$y = y_1 + y_2 = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

(NOT x_1) AND (NOT x_2) OR x_1 AND x_2

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{x_1} \cdot \overline{x_2}$$

$$x_1 \cdot x_2$$

$$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables

Instead of writing expressions as sum of terms that make y equal to 1, we can also write expressions using terms that make y equal to 0

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$
$$y = \overline{x_1 \cdot x_2}$$

Here we are telling when y will be true

FALSE when both are true

Here we are telling when y will be false

$$y = \overline{x_1} + \overline{x_2}$$

Recall

$$\overline{x_1} + \overline{x_2} = \overline{x_1 \cdot x_2}$$

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables


x_1	x_2	y	
0	0	0	$x_1 + x_2$
0	1	1	
1	0	1	
1	1	0	$\overline{x_1} + \overline{x_2}$

$y = (x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$

Product of Sum (POS) form

Digital Design

System Description

 

Truth Table

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Boolean Expression

$$f = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

**Minimized
Boolean Expression**

$$\Rightarrow f = z$$


Gate Netlist

Calculation using Digital System

- Binary signals represent logic states
 - can implement any logic
 - logic consists of AND, OR & NOT condition
 - Boolean Algebra
- Binary signals can represent any numbers
 - We can do all arithmetic over it
 - Enables any calculations
 - Addition, Subtraction, Multiplication, Division, etc.
- Computers can do calculations
 - evaluate logic states and make decision over that

How to do such
calculations?

Modular Approach

 

There are certain sub-systems or blocks that are used quite often such as :

1. Adder/Subtractors, Multipliers
2. Decoders, Encoders
3. Multiplexers, Demultiplexers
4. Comparators
5. Parity Generators

Binary Addition

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 1 \quad 0 \\ \hline 0 \quad 1 \\ \hline 1 \quad 1 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 1 \ 0 \end{array}$$


$$\begin{array}{r} 1 \\ 1 \\ \hline 1 \\ \hline 1 \ 1 \end{array}$$

$$\begin{array}{r} 1 \ 0 \ 1 \\ \hline 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 1 \ 1 \end{array}$$
 
$$\begin{array}{r} 1 \ 1 \ 0 \ 1 \\ + \ 1 \ 1 \ 1 \ 0 \\ \hline 1 \ 1 \ 0 \ 1 \ 1 \end{array}$$



1 bit Addition: Half Adder

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

Boolean Expression

 

Gate level
implementation





Why a Modular Approach?

- Let us make a 2 bit adder circuit which can add two 2-bit numbers

$$\begin{array}{r} x_1 \ x_0 \\ + \ y_1 \ y_0 \\ \hline z_2 \ z_1 \ z_0 \end{array}$$

- There are 4 inputs and 3 outputs
- Let us write down all possible combinations!
 - $2^4 = 16$ rows in the truth table
- Write down Boolean expressions and design implementation?
- What about 3 bits?
- ❑ Let us take the modular approach


Adder: First bit

    

Truth Table


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

 

Implementation

Adder: Second bit

 

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 1 \\ \hline 0 \\ \hline 1 \end{array} \quad \begin{array}{r} 0 \\ \hline 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 1 \ 0 \end{array}$$

But there can be carry
from previous bits.


$$\begin{array}{r} 1 \\ x_1 \ 1 \\ + \ y_1 \ 1 \\ \hline z_2 \ z_1 \ 0 \end{array}$$

Single Bit Full Adder

 


$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$

$$C = x.y + x.z + y.z$$

 


a	b	c	S	CY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Adder: Half Adder vs Full adder

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

¹
 1 1 1
 1 1 0

 1 1 0 1

 

a	b	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in};$$

$$C_{out} = \bar{a}.b.c_{in} + a.\bar{b}.c_{in} + a.b.\bar{c}_{in} + a.b.c_{in}$$


Full Adder Circuit using Half Adders

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}$$


$$S = C_{in} \oplus (a \oplus b)$$

$$C_{out} = \bar{a}.b.C_{in} + a.\bar{b}.C_{in} + a.b.\bar{C}_{in} + a.b.C_{in}$$
 
$$C_{out} = C_{in}(a.\bar{b} + \bar{a}.b) + a.b = C_{in}.(a \oplus b) + a.b$$



Multi-bit Adder

 


$$\begin{array}{r} x_1 \quad x_0 \\ + \quad y_1 \quad y_0 \\ \hline z_2 \quad z_1 \quad z_0 \end{array}$$

Multi-bit Adder

- How to add two 4-bit numbers?
- Truth table would have $2^8=256$ entries
- Instead, use already designed logic circuits as subsystems
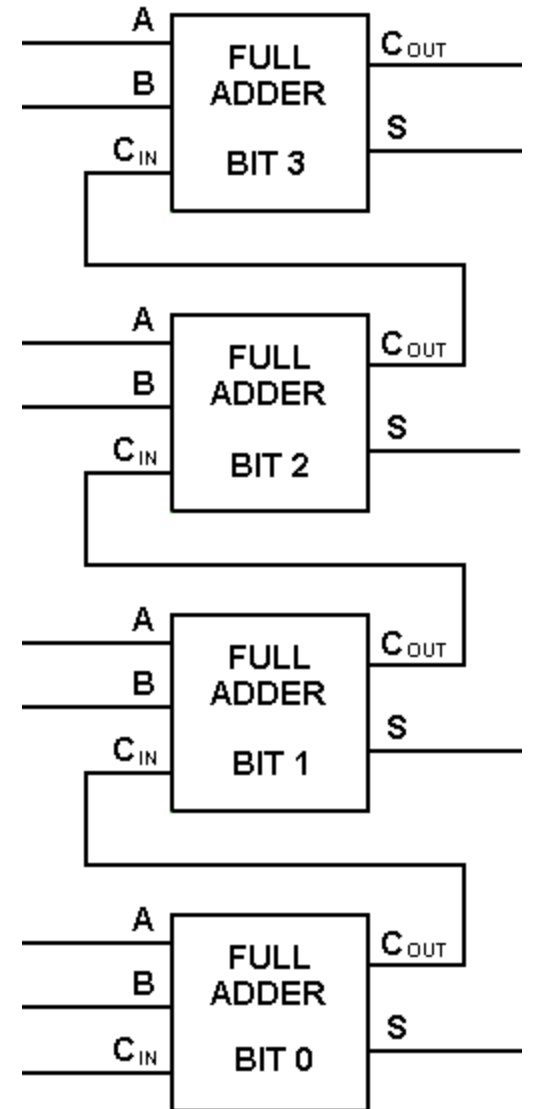
$$\begin{array}{r} 1101 \\ + 1110 \\ \hline 11011 \end{array}$$



Addition/Subtraction Computation

$$\begin{array}{r} +5 \\ +2 \\ \hline +7 \end{array}$$

$$\begin{array}{r} 0101 \\ +0010 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} -5 \\ +2 \\ \hline -3 \end{array}$$

$$\begin{array}{r} 1011 \\ +0010 \\ \hline 1101 \end{array}$$

2's complement is 0011 = 3

$$\begin{array}{r} +5 \\ -2 \\ \hline +3 \end{array}$$


$$\begin{array}{r} 0101 \\ +1110 \\ \hline 0011 \end{array}$$

$$\begin{array}{r} -5 \\ -2 \\ \hline -7 \end{array}$$

$$\begin{array}{r} 1011 \\ +1110 \\ \hline 1001 \end{array}$$

2's complement is 0111 = 7

Answer is in 2's complement form

 

Overflow

- Take care to detect overflow when adding

$$\begin{array}{r} + 5 \quad \quad 00101 \\ + 13 \quad \quad 01101 \\ \hline + 18 \quad \quad \color{red}{0}10010 \end{array}$$


After discarding the final carry $\color{red}{0}$,
2's complement of 10010 is 01110 = $(14)_{10}$
We get a wrong answer!

- Sum of positive numbers = negative
- Sum of negative numbers = positive

} overflow


August 2016: Casino machine at Resorts World Casino printed a prize ticket of \$42,949,672.76 as a result of an overflow bug. The Casino refused to pay this amount calling it a malfunction. The Iowa Supreme Court ruled in favor of the Casino.

4-bit Adder

 

$A_3 A_2 A_1 A_0$	$B_3 B_2 B_1 B_0$	$S_3 S_2 S_1 S_0$	C_{out}
0000	0000	0000	0
0000	0001	0001	0
0001	0000	0001	0
⋮	⋮	⋮	⋮
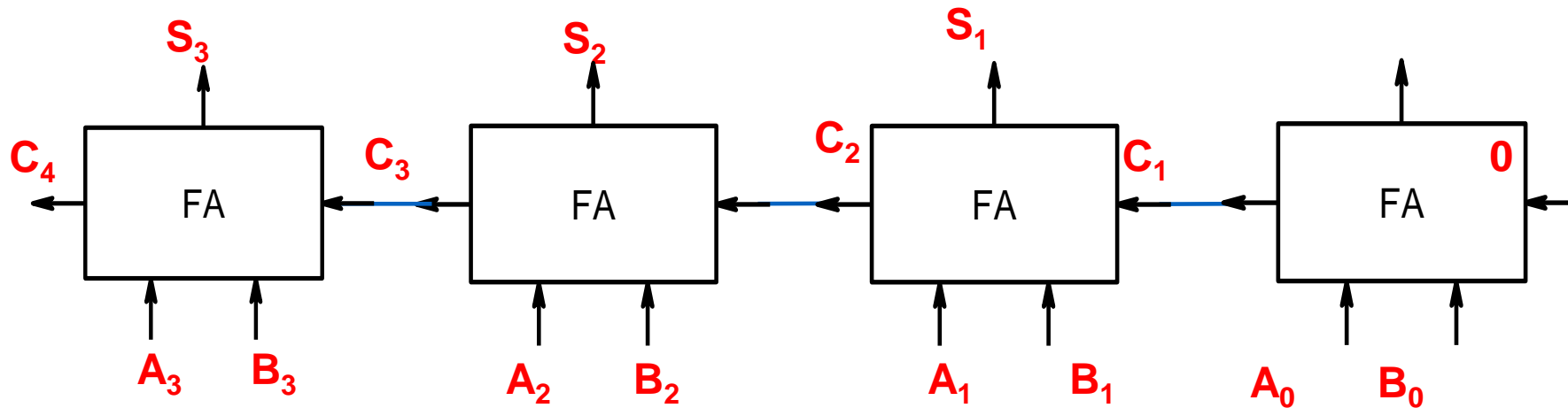
$$\begin{array}{r}
 C_3 C_2 C_1 \\
 A_3 A_2 A_1 A_0 \\
 B_3 B_2 B_1 B_0 \\
 \hline
 C_4 S_3 S_2 S_1 S_0
 \end{array}$$




4-bit Subtractor

$$A - B = A + 2\text{'s complement of } B$$


$$A - B = A + 1\text{'s complement of } B + 1$$

$$A - B = A + \overline{B} + 1$$

 

$$B_0 \oplus 1 = B_0 \cdot \overline{1} + \overline{B_0} \cdot 1 = \overline{B_0}$$

4-bit Adder and Subtractor

 

$$B_0 \oplus 0 = B_0 \cdot \bar{0} + \bar{B}_0 \cdot 0 = B_0$$

$$B_0 \oplus 1 = B_0 \cdot \bar{1} + \bar{B}_0 \cdot 1 = \bar{B}_0$$

$M = 0$ for Adder

$M = 1$ for Subtractor