

# ESC201: Lecture 16




**Dr. Imon Mondal**

ASSISTANT PROFESSOR,  
ELECTRICAL ENGINEERING, IIT KANPUR


# Digital Circuits

## Combinational Circuits

 


Output is determined by current values of inputs only.


## Sequential Circuits

 

 Output is determined in general by current values of inputs and past values of inputs/outputs as well.




# Memory with Set/Reset Knob

 

Two memory states are possible:


1.  $Q1=Q3=0$  (Low),  $Q2=1$  (High)
2.  $Q1=Q3=1$  (High),  $Q2=0$  (Low)

But how will one change the state?

 


We need at least 2 i/p logic gates

 - NOR gate behave like INV if one i/p is 0
- NAND behaves like INV if one i/p is 1




NOR-based SR Latch

 

NAND-based SR Latch

# Set-Reset (SR) Latch: Set State

 


$Q = 1; \bar{Q} = 0$  Set State

$Q = 0; \bar{Q} = 1$  Reset State

$$\overline{1 + Q} = 0$$

S	R	Q	$\bar{Q}$	State
1	0	1	0	SET

# Set-Reset (SR) Latch: Reset State

 


$Q = 1; \bar{Q} = 0$  Set State

$Q = 0; \bar{Q} = 1$  Re set State


$$\overline{1 + \bar{Q}} = 0$$

S	R	Q	$\bar{Q}$	State
1	0	1	0	SET
0	1	0	1	RESET

# SR Latch: 'Hold' (memory)

 


S	R	Q	$\bar{Q}$	State
1	0	1	0	SET
0	0	1	0	HOLD


 


S	R	Q	$\bar{Q}$	State
1	0	1	0	SET
0	0	1	0	HOLD
0	1	0	1	RESET
0	0	0	1	HOLD
 
# SR Latch: Invalid Input and Gate Delays






Suppose gate-1 is faster

  

   **Q = 1**


On the other hand suppose that gate-2 is faster.




**Again the output is unpredictable in general**



# NOR-based vs NAND-based SR Latch


 


S	R	Q	$\bar{Q}$	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	$\bar{Q}$	HOLD
1	1	0	0	INVALID

 


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	$\bar{Q}$	HOLD
0	0	1	1	INVALID

# NAND-based SR Latch with Enable

  


Enable	S	R	Q	$\bar{Q}$	State
0	x	x	Q	$\bar{Q}$	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	$\bar{Q}$	Hold
1	1	1	0	0	Invalid

## D latch

 

Enable	S	R	Q	$\bar{Q}$	State
0	x	x	Q	$\bar{Q}$	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	$\bar{Q}$	Hold
1	1	1	0	0	Invalid

 

If  $EN = 1$  then  $Q = D$  otherwise the latch is in Hold state

# Synchronous Sequential Circuits

