

ESC201: Lecture 13



Dr. Imon Mondal

ASSISTANT PROFESSOR,
ELECTRICAL ENGINEERING, IIT KANPUR

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{x_1} \cdot \overline{x_2}$$

$$x_1 \cdot x_2$$

$$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables

Instead of writing expressions as sum of terms that make y equal to 1, we can also write expressions using terms that make y equal to 0

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$
$$y = \overline{x_1 \cdot x_2}$$

Here we are telling when y will be true

FALSE when both are true

Here we are telling when y will be false

$$y = \overline{x_1} + \overline{x_2}$$

Recall

$$\overline{x_1} + \overline{x_2} = \overline{x_1 \cdot x_2}$$

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables


x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = (x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$$

$(x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$
Product of Sum (POS) form

Digital Design

System Description

 

Truth Table

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Boolean Expression


$$f = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

**Minimized
Boolean Expression**

$$\Rightarrow f = z$$

Gate Netlist

Modular Approach

 

There are certain sub-systems or blocks that are used quite often such as :

1. Adder/Subtractors, Multipliers
2. Decoders, Encoders
3. Multiplexers, Demultiplexers
4. Comparators
5. Parity Generators

Binary Addition

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 1 \quad 0 \\ \hline 0 \quad 1 \\ \hline 1 \quad 1 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 1 \ 0 \end{array}$$


$$\begin{array}{r} 1 \\ 1 \\ \hline 1 \\ \hline 1 \ 1 \end{array}$$

$$\begin{array}{r} 1 \ 0 \ 1 \\ \hline 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 1 \ 1 \end{array}$$
 
$$\begin{array}{r} 1 \ 1 \ 0 \ 1 \\ + \ 1 \ 1 \ 1 \ 0 \\ \hline 1 \ 1 \ 0 \ 1 \ 1 \end{array}$$



Addition

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table


$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

How to get this expression?

How to get this gate implementation?

 

 How to get an expression from truth table?



x_1	x_2	y
0	0	0
0	1	1
1	0	0
1	1	0

$y = 1$ when x_1 is 0 and x_2 is 1

Boolean expression

$$y = \overline{x_1} \cdot x_2$$

(NOT x_1) AND x_2

How to get an expression from truth table?

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	0

$y = \overline{x_1} \cdot \overline{x_2}$

x_1	x_2	y
0	0	0
0	1	0
1	0	1
1	1	0

$y = x_1 \cdot \overline{x_2}$

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$

$$y = y_1 + y_2 = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

(NOT x_1) AND (NOT x_2) OR x_1 AND x_2

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{x_1} \cdot \overline{x_2}$$

$$x_1 \cdot x_2$$

$$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables

Instead of writing expressions as sum of terms that make y equal to 1, we can also write expressions using terms that make y equal to 0

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$
$$y = \overline{x_1 \cdot x_2}$$

Here we are telling when y will be true

FALSE when both are true

Here we are telling when y will be false

$$y = \overline{x_1} + \overline{x_2}$$

Recall

$$\overline{x_1} + \overline{x_2} = \overline{x_1 \cdot x_2}$$

Boolean Expressions & Truth Tables

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

Sum of Products (SOP) form

Boolean Expressions & Truth Tables


x_1	x_2	y	
0	0	0	$x_1 + x_2$
0	1	1	
1	0	1	
1	1	0	$\overline{x_1} + \overline{x_2}$

$y = (x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$

Product of Sum (POS) form

Digital Design

System Description

 

Truth Table

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Boolean Expression

$$f = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

**Minimized
Boolean Expression**

$$\Rightarrow f = z$$


Gate Netlist

Calculation using Digital System

- Binary signals represent logic states
 - can implement any logic
 - logic consists of AND, OR & NOT condition
 - Boolean Algebra
- Binary signals can represent any numbers
 - We can do all arithmetic over it
 - Enables any calculations
 - Addition, Subtraction, Multiplication, Division, etc.
- Computers can do calculations
 - evaluate logic states and make decision over that

How to do such
calculations?

Modular Approach

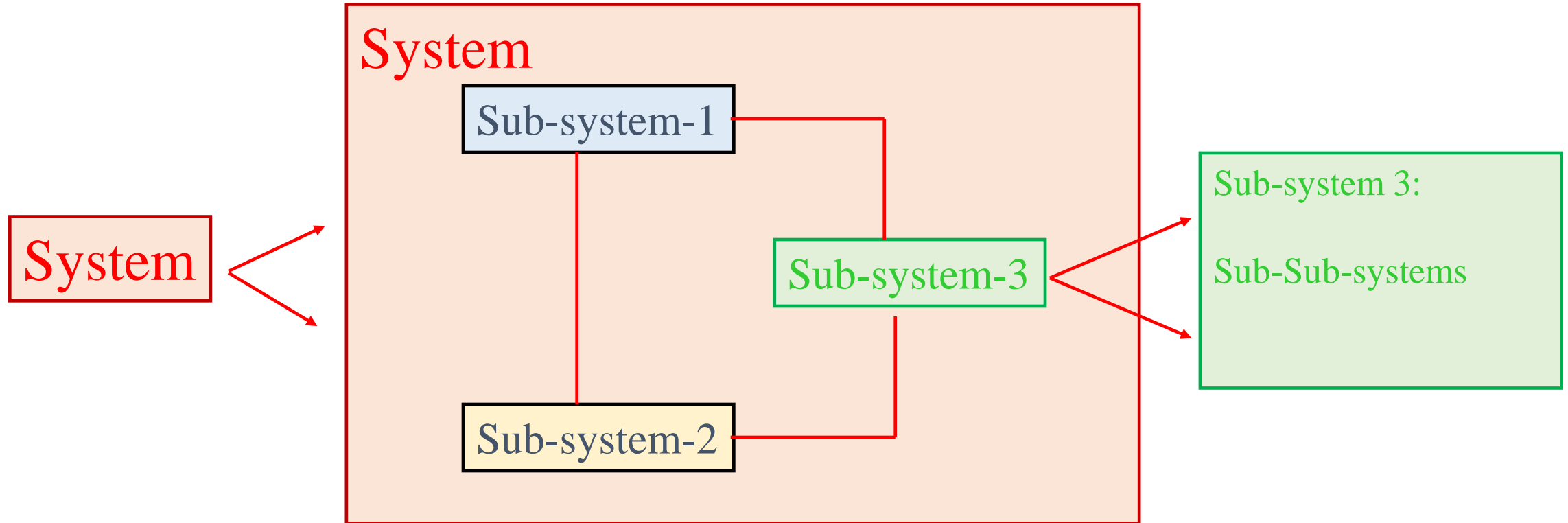

There are certain sub-systems or blocks that are used quite often such as :

1. Adder/Subtractors, Multipliers
2. Decoders, Encoders
3. Multiplexers, Demultiplexers
4. Comparators
5. Parity Generators

Binary Addition

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 1 \quad 0 \\ \hline 0 \quad 1 \\ \hline 1 \quad 1 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 1 \ 0 \end{array}$$


$$\begin{array}{r} 1 \\ 1 \\ \hline 1 \\ \hline 1 \ 1 \end{array}$$

$$\begin{array}{r} 1 \ 0 \ 1 \\ \hline 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 1 \ 1 \end{array}$$
 
$$\begin{array}{r} 1 \ 1 \ 0 \ 1 \\ + \ 1 \ 1 \ 1 \ 0 \\ \hline 1 \ 1 \ 0 \ 1 \ 1 \end{array}$$



1 bit Addition: Half Adder

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

Boolean Expression

 

Gate level
implementation





Why a Modular Approach?

- Let us make a 2 bit adder circuit which can add two 2-bit numbers

$$\begin{array}{r} x_1 \ x_0 \\ + \ y_1 \ y_0 \\ \hline z_2 \ z_1 \ z_0 \end{array}$$

- There are 4 inputs and 3 outputs
- Let us write down all possible combinations!
 - $2^4 = 16$ rows in the truth table
- Write down Boolean expressions and design implementation?
- What about 3 bits?
- ❑ Let us take the modular approach


Adder: First bit

    

Truth Table


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

 

Implementation

Adder: Second bit

 

$$\begin{array}{r} 0 \\ \hline 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 1 \\ \hline 0 \\ \hline 1 \end{array} \quad \begin{array}{r} 0 \\ \hline 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ \hline 1 \\ \hline 1 \ 0 \end{array}$$

But there can be carry
from previous bits.


$$\begin{array}{r} 1 \\ x_1 \ 1 \\ + \ y_1 \ 1 \\ \hline z_2 \ z_1 \ 0 \end{array}$$

Single Bit Full Adder

 


$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$

$$C = x.y + x.z + y.z$$

 


a	b	c	S	CY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Adder: Half Adder vs Full adder

 


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

¹
 1 1 1
 1 1 0

 1 1 0 1

 

a	b	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in};$$

$$C_{out} = \bar{a}.b.c_{in} + a.\bar{b}.c_{in} + a.b.\bar{c}_{in} + a.b.c_{in}$$


Full Adder Circuit using Half Adders

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}$$


$$S = C_{in} \oplus (a \oplus b)$$

$$C_{out} = \bar{a}.b.C_{in} + a.\bar{b}.C_{in} + a.b.\bar{C}_{in} + a.b.C_{in}$$
 
$$C_{out} = C_{in}(a.\bar{b} + \bar{a}.b) + a.b = C_{in}.(a \oplus b) + a.b$$



Multi-bit Adder

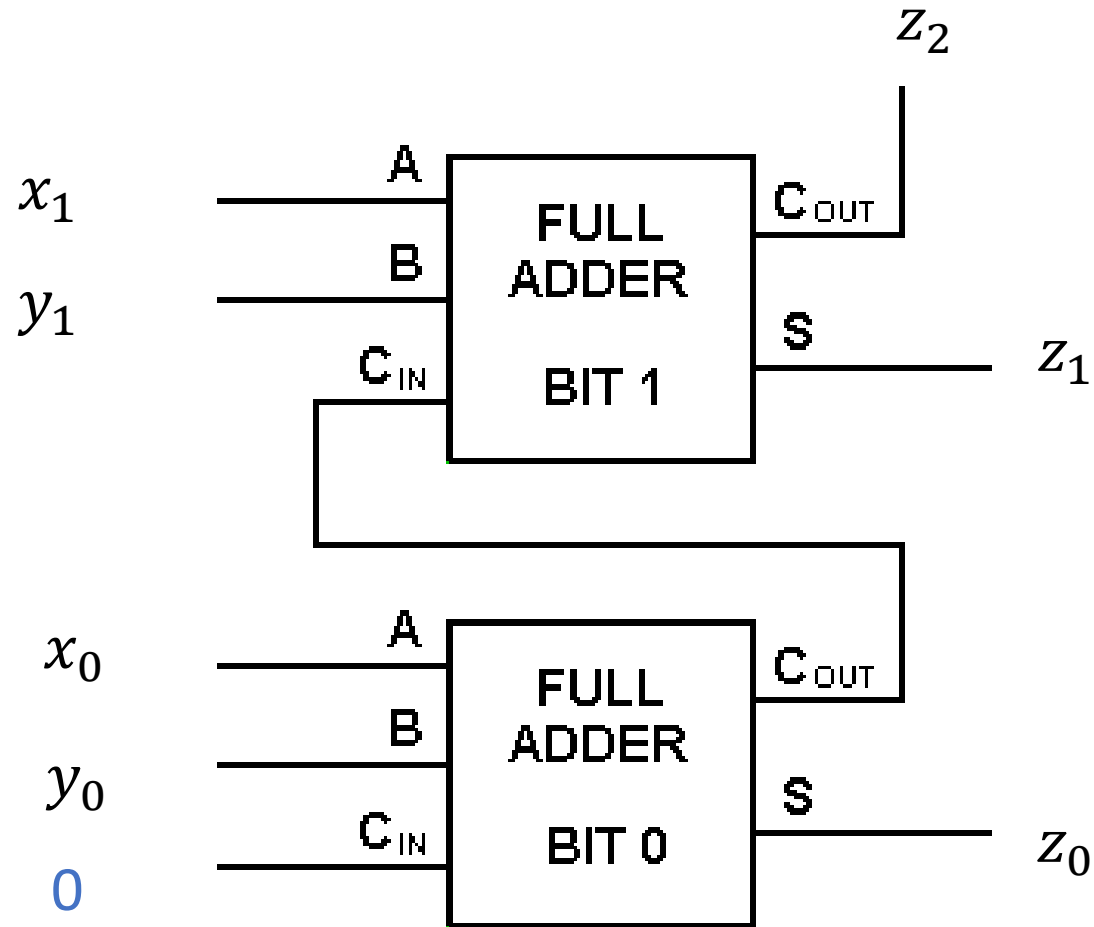


$$\begin{array}{r} x_1 \quad x_0 \\ + \quad y_1 \quad y_0 \\ \hline z_2 \quad z_1 \quad z_0 \end{array}$$

Multi-bit Adder

- How to add two 4-bit numbers?
- Truth table would have $2^8=256$ entries
- Instead, use already designed logic circuits as subsystems
 
$$\begin{array}{r} 1101 \\ + 1110 \\ \hline 11011 \end{array}$$



Addition/Subtraction Computation

$$\begin{array}{r} +5 \\ +2 \\ \hline +7 \end{array}$$

$$\begin{array}{r} 0101 \\ +0010 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} -5 \\ +2 \\ \hline -3 \end{array}$$

$$\begin{array}{r} 1011 \\ +0010 \\ \hline 1101 \end{array}$$

2's complement is 0011 = 3

$$\begin{array}{r} +5 \\ -2 \\ \hline +3 \end{array}$$


$$\begin{array}{r} 0101 \\ +1110 \\ \hline 0011 \end{array}$$

$$\begin{array}{r} -5 \\ -2 \\ \hline -7 \end{array}$$

$$\begin{array}{r} 1011 \\ +1110 \\ \hline 1001 \end{array}$$

2's complement is 0111 = 7

Answer is in 2's complement form

 

Overflow

- Take care to detect overflow when adding


$$\begin{array}{r} + 5 \quad \quad 00101 \\ + 13 \quad \quad 01101 \\ \hline + 18 \quad \quad \textcolor{red}{0}10010 \end{array}$$

After discarding the final carry **0**,
2's complement of 10010 is 01110 = $(14)_{10}$
We get a wrong answer!

- Sum of positive numbers = negative
- Sum of negative numbers = positive


} overflow

4-bit Adder

 

$A_3 A_2 A_1 A_0$	$B_3 B_2 B_1 B_0$	$S_3 S_2 S_1 S_0$	C_{out}
0000	0000	0000	0
0000	0001	0001	0
0001	0000	0001	0
⋮	⋮	⋮	⋮
 
$$\begin{array}{r}
 C_3 C_2 C_1 \\
 A_3 A_2 A_1 A_0 \\
 B_3 B_2 B_1 B_0 \\
 \hline
 C_4 S_3 S_2 S_1 S_0
 \end{array}$$




4-bit Subtractor

$$A - B = A + 2\text{'s complement of } B$$

$$A - B = A + 1\text{'s complement of } B + 1$$

$$A - B = A + \overline{B} + 1$$

 


Handwritten notes in red:

- $x_1 = 1$
- $x_2 = 1$
- $x_2 = 0$
- x_1

$$B_0 \oplus 1 = B_0 \cdot \overline{1} + \overline{B_0} \cdot 1 = \overline{B_0}$$

4-bit Adder and Subtractor

 


$$B_0 \oplus 0 = B_0 \cdot \bar{0} + \bar{B}_0 \cdot 0 = B_0$$

$$B_0 \oplus 1 = B_0 \cdot \bar{1} + \bar{B}_0 \cdot 1 = \bar{B}_0$$

$M = 0$ for Adder

$M = 1$ for Subtractor

Multiplexers (MUX)

 


S	y
0	I ₀
1	I ₁

is a shortcut to say

$$y = \bar{S} I_0 + S I_1$$


S	I ₀	I ₁	y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

$$\begin{aligned}
 y &= \bar{S} I_0 \bar{I}_1 + \bar{S} I_0 I_1 + S \bar{I}_0 I_1 + S I_0 I_1 \\
 &= \bar{S} I_0 (\bar{I}_1 + I_1) + S I_1 (\bar{I}_0 + I_0) \\
 &= \bar{S} I_0 + S I_1
 \end{aligned}$$


- The shortcut version of truth table is more useful
- => Minimization is more natural

Bigger Multiplexers

 


S_1	S_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
 
$$y = \overline{S_1} \overline{S_0} I_0 + \overline{S_1} S_0 I_1 + S_1 \overline{S_0} I_2 + S_1 S_0 I_3$$





Bigger MUX from Smaller MUX


S	y
0	I ₀
1	I ₁

 

S ₁	S ₀	y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

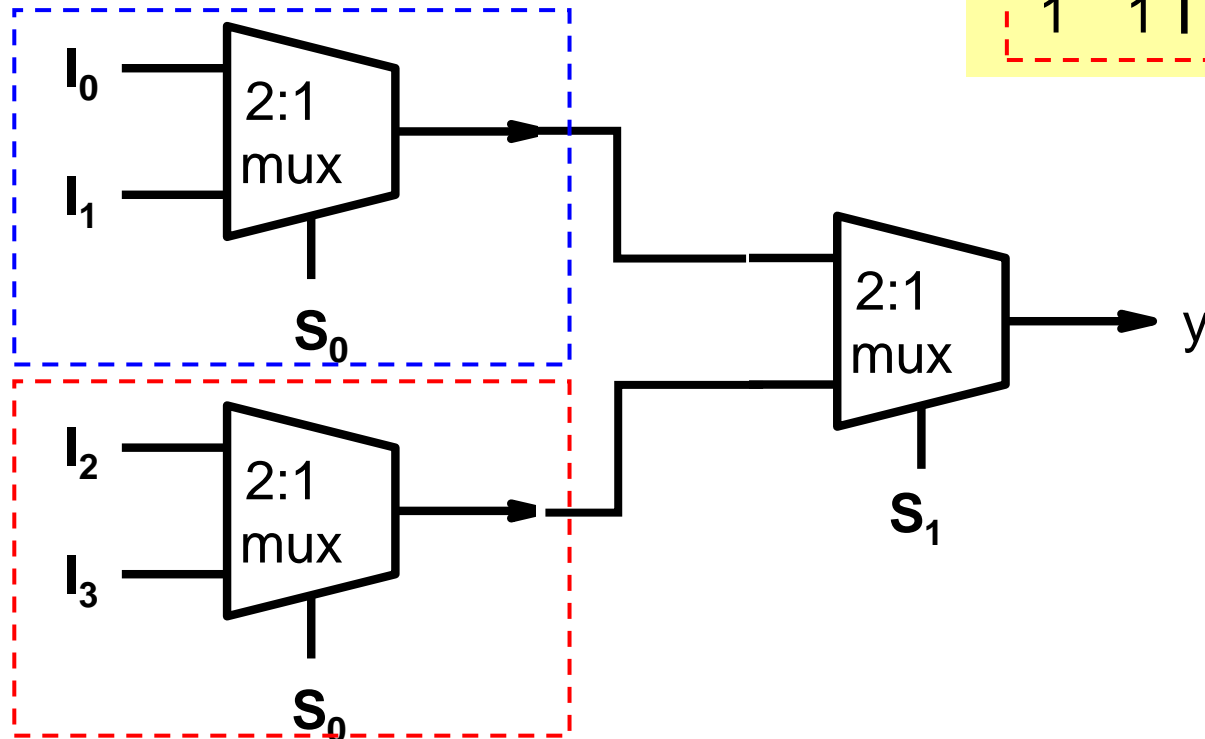 


Bigger MUX from Smaller MUX with Enable

 


E	S	y
0	x	0
1	0	I_0
1	1	I_1

S_1	S_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Implementation of a Function using Mux

 A 2 variable function can be implemented with a 4:1 mux with 2 select lines: **one-to-one correspondence**




Can we do better?

Implementation of a Function using Mux

A 2 variable function can be implemented with a 2:1 mux with 1 select line
 
$$y = x_1 \overline{x_2} + \overline{x_1} x_2$$




x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$y = x_2$ when $x_1 = 0$

$y = \overline{x_2}$ when $x_1 = 1$


Implementation of a Function using Mux

 A 3 variable function can be implemented with a 4:1 mux with 2 select lines



Implementation of a Function using Mux

 A 3 variable function can be implemented with a 4:1 mux with 2 select lines: **not an unique implementation**



x	y	z	F
0	0	0	0
1	0	0	0
0	0	1	1
1	0	1	0
0	1	0	1
1	1	0	1
0	1	1	0
1	1	1	1

F = 0 when yz = 00


F = \bar{x} when yz = 01

F = 1 when yz = 10

F = x when yz = 11

Mux Applications


Resource Sharing

 

S_1	S_0	$y =$
0	0	$a+c$
0	1	$a+d$
1	0	$b+c$
1	1	$b+d$

Decoders

 
- Decodes an encoded information
 - maps a smaller number of inputs to a larger set of outputs



B	A	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


$$\begin{aligned}Y_0 &= \overline{B} \cdot \overline{A}; \\Y_1 &= \overline{B} \cdot A; \\Y_2 &= B \cdot \overline{A}; \\Y_3 &= B \cdot A\end{aligned}$$

Decoders with 'Enable' input


 


E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
 
$$Y_0 = E \cdot \bar{B} \cdot \bar{A} ; Y_1 = E \cdot \bar{B} \cdot A ; Y_2 = E \cdot B \cdot \bar{A} ; Y_3 = E \cdot B \cdot A$$




Decoders in Vending Machine

 
 


Term Generator for SOP Expression of a Function

x	y	term
0	0	$\overline{x} \cdot \overline{y}$
0	1	$\overline{x} \cdot y$
1	0	$x \cdot \overline{y}$
1	1	$x \cdot y$

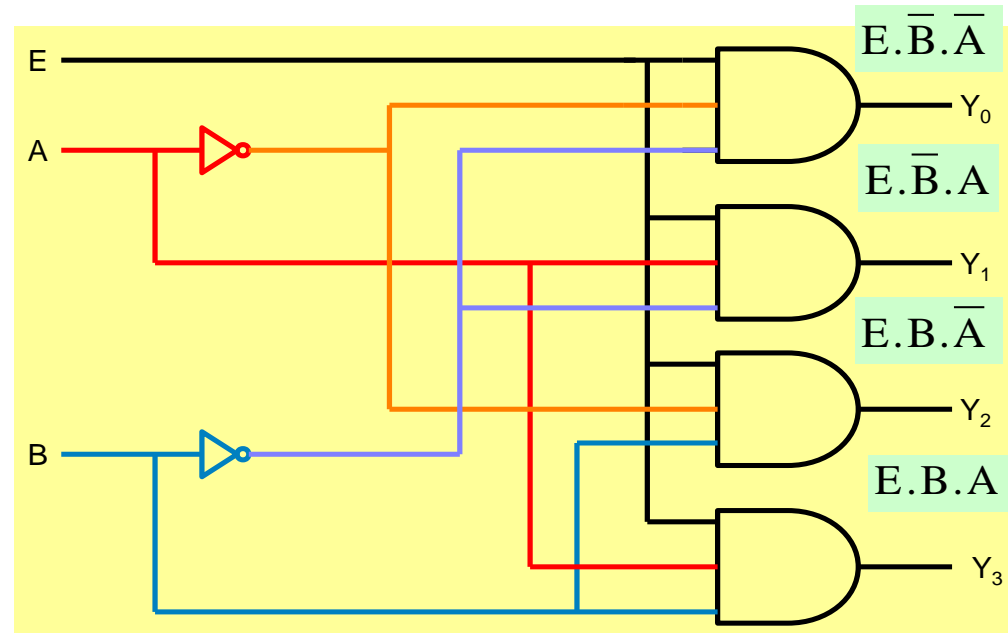


B	A	f_1
0	0	0
0	1	1
1	0	1
1	1	0

  

Implementation of a Function using Decoders

- Decoder allows a quick implementation
- No minimization, but lots of gates...


C	B	A	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

 



Bigger Decoders

- 3 by 8 decoder using a 2 by 4 decoder

e	c	b	a	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1


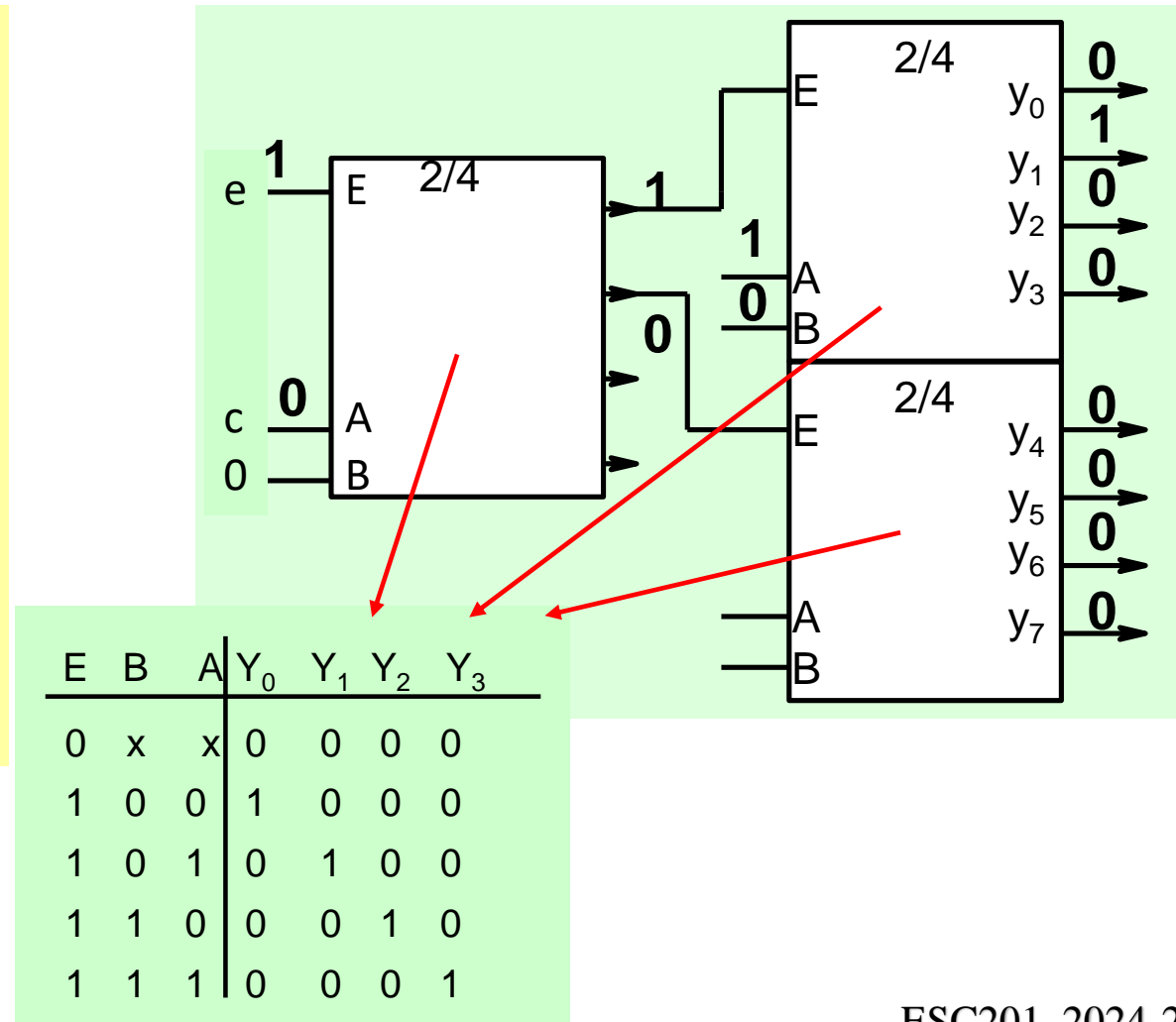


De-Multiplexer

  

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

De-Mux vs Decoder

 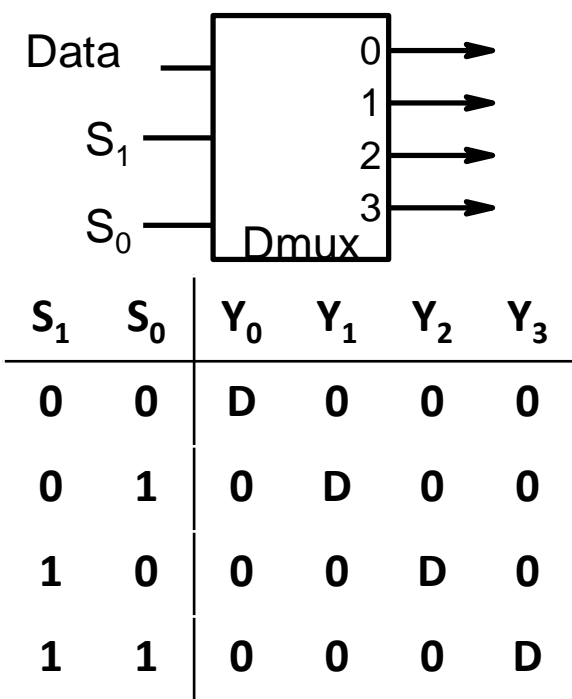

E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Only difference is in name and application

