

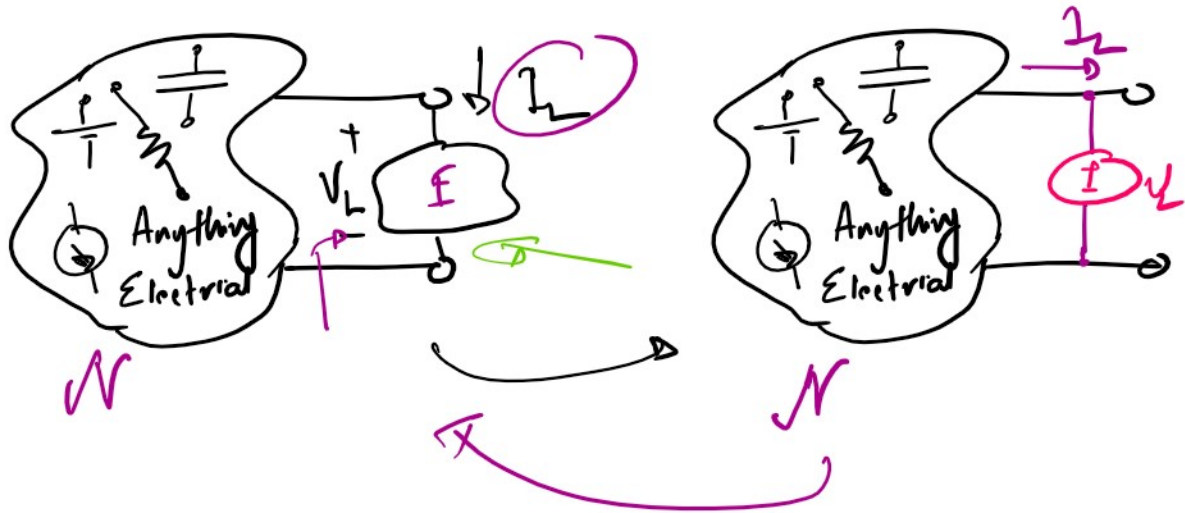




SUBSTITUTION THEOREM

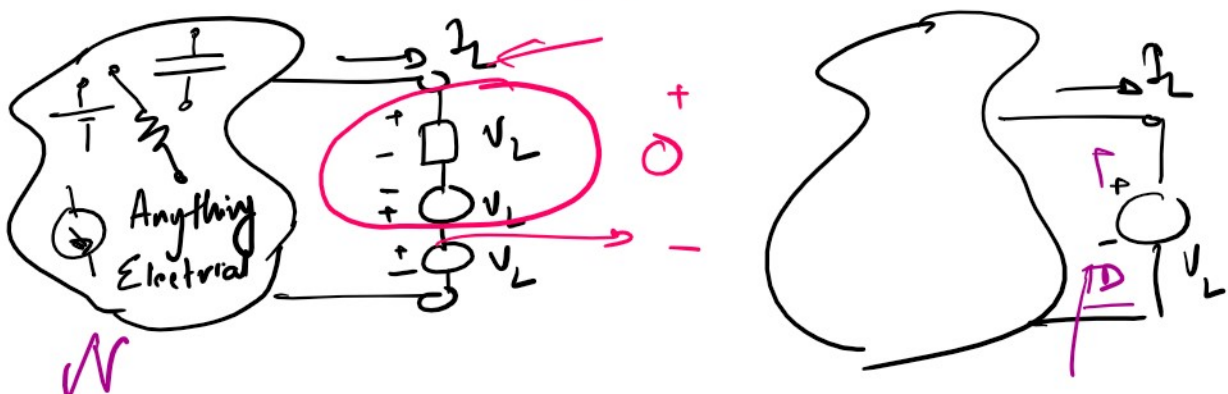



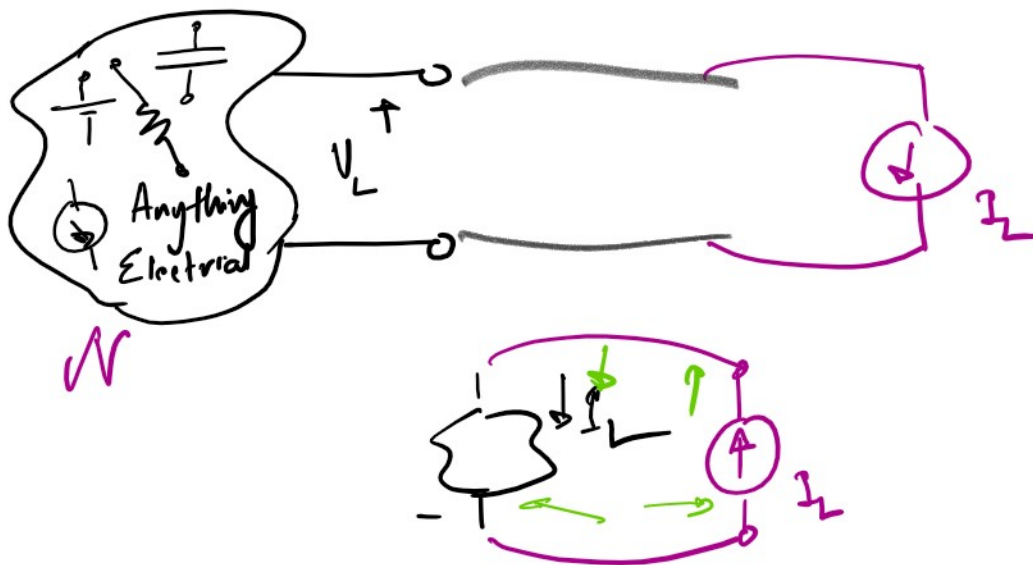
If an element is replaced by a voltage source with the same voltage or a current source with the same current, the rest of the circuit remains unchanged.



SOURCE TRANSFORMATION

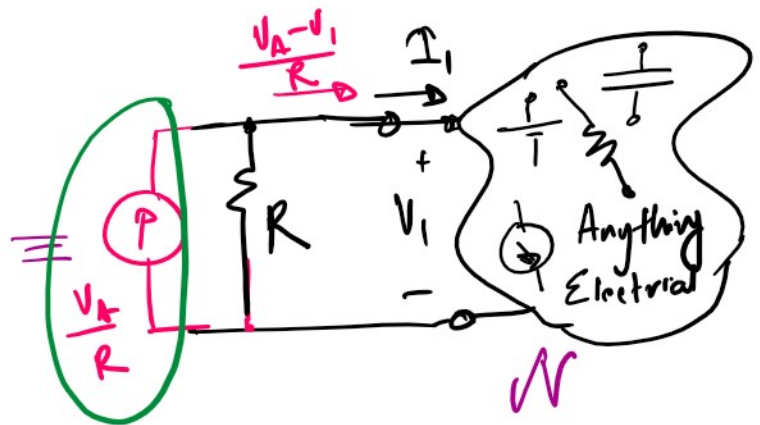
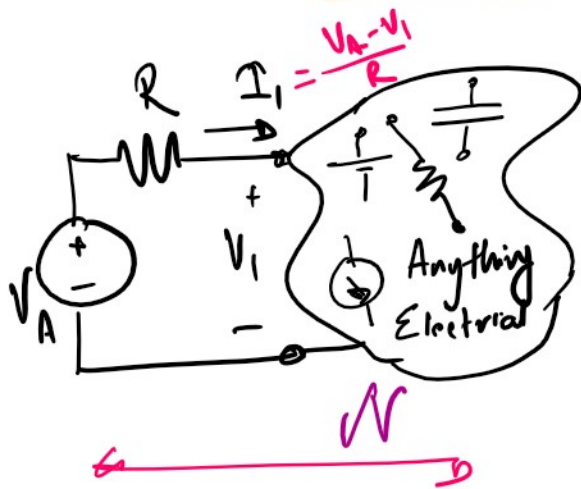

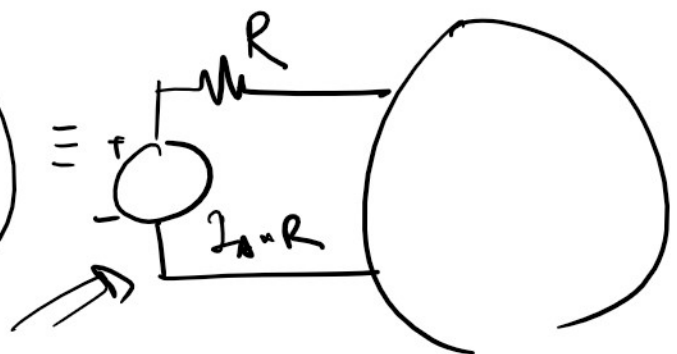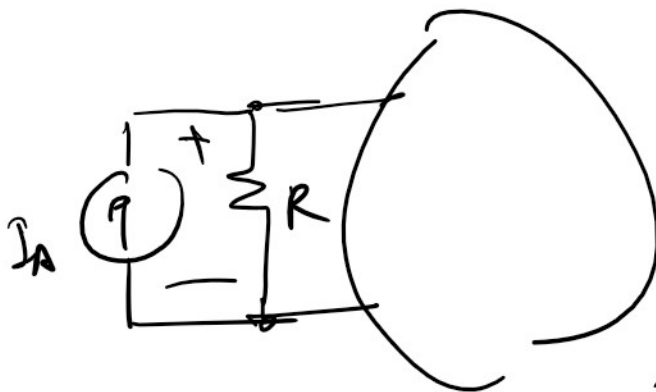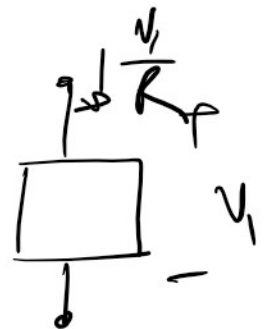
$$I_1 = \frac{V_A - V_1}{R} = \left(\frac{V_A}{R} \right) - \left(\frac{V_1}{R} \right)$$




EQUIVALENT

RESISTANCE

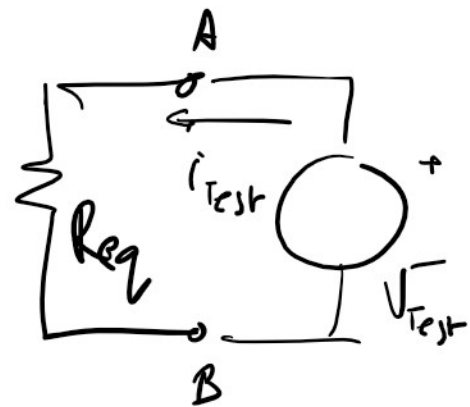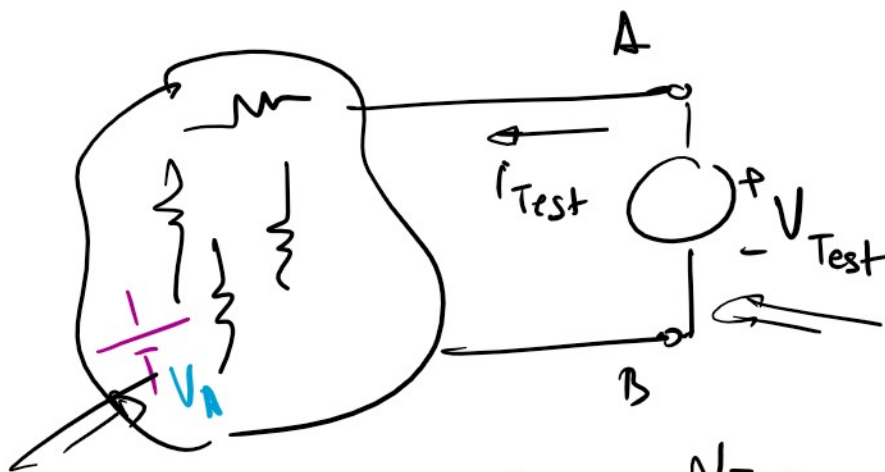


$$R_{eq} = \frac{V_{Test}}{i_{Test}}$$
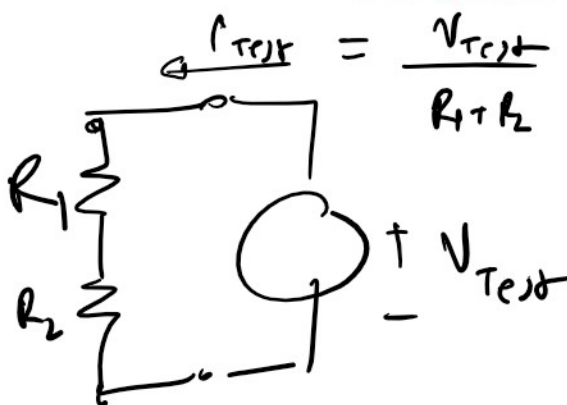
$$i_{Test} = \alpha V_{Test} + \cancel{A V_A}$$





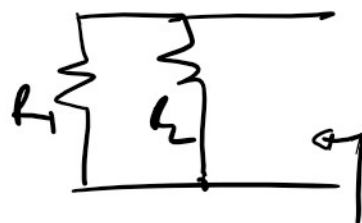
$$\Rightarrow R_{eq} = \frac{V_{Test}}{i_{Test}} = R_1 + R_2$$



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

THEVENIN'S THEOREM


THEVENIN'S THEOREM

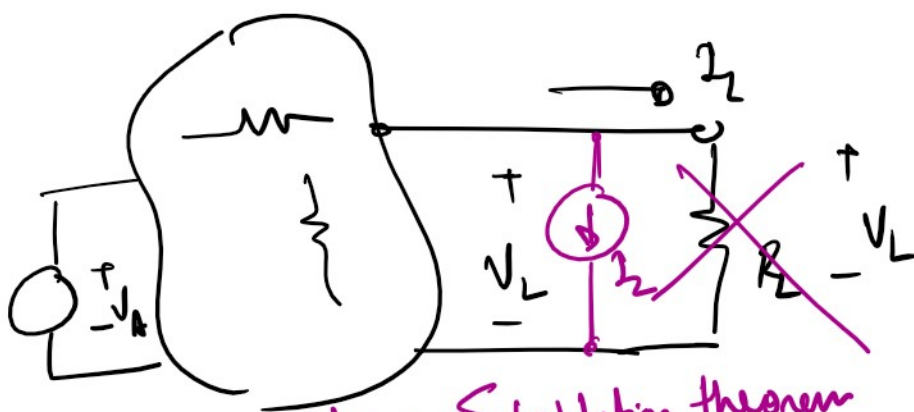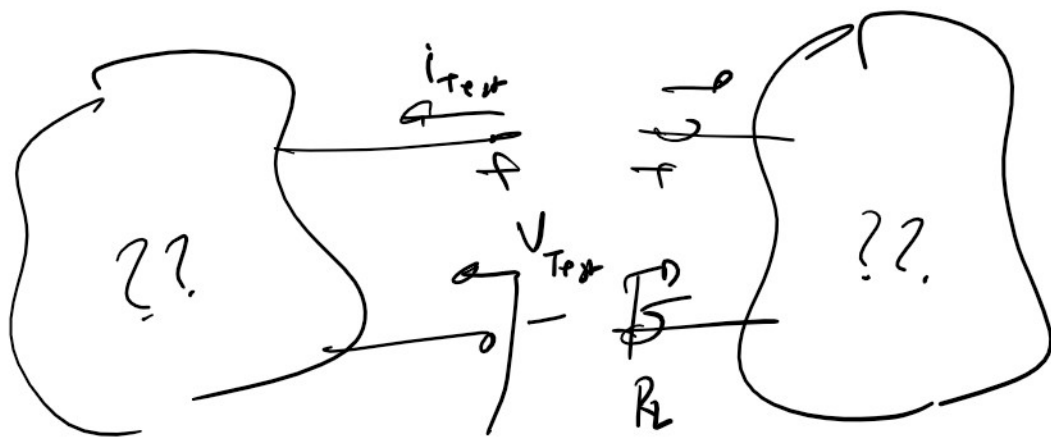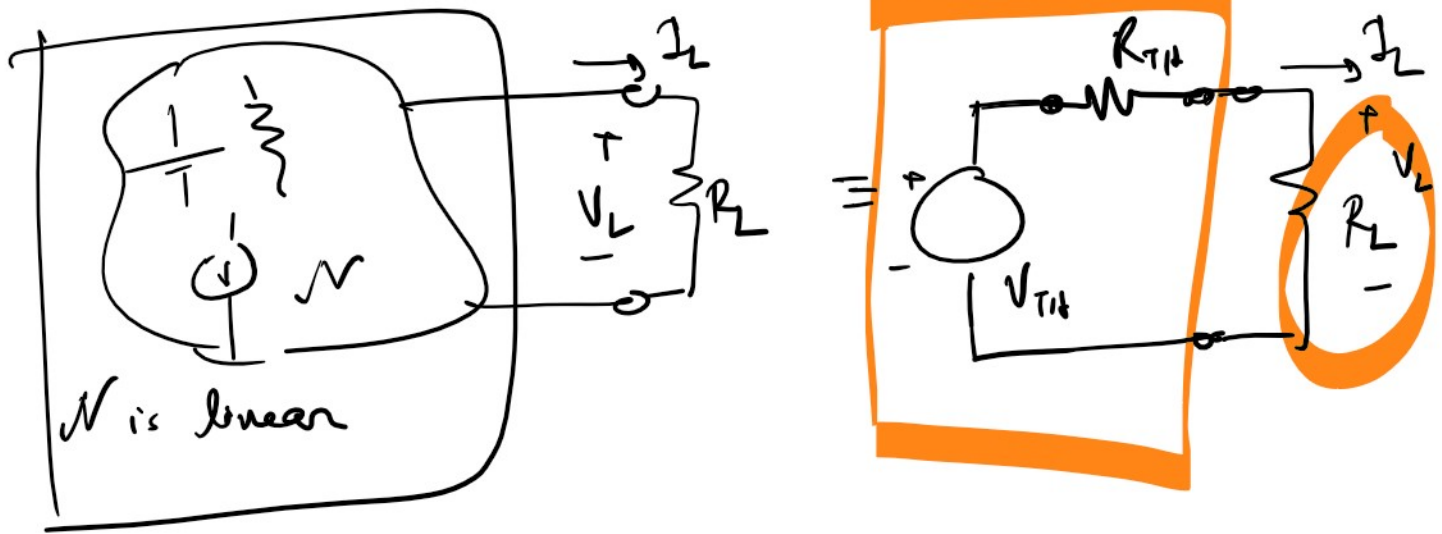


Using Substitution theorem

$$V_L = I_L R_L$$

$$I_L = \frac{V_L}{R_L}$$

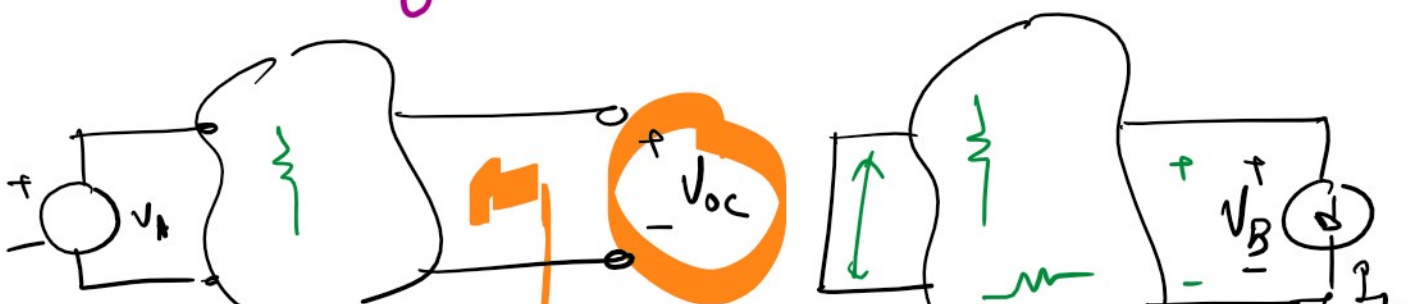


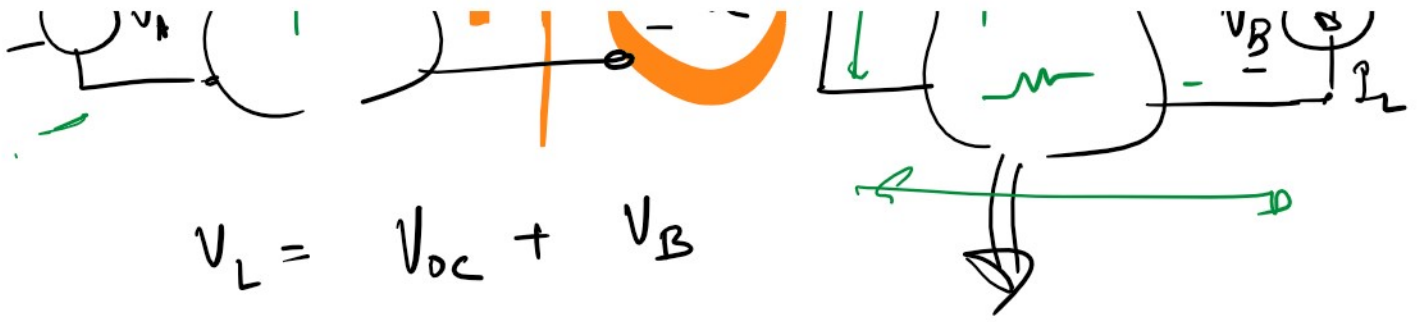

$$V_L = V_{oc} + V_B$$

$$= V_{oc} - R_{eq} I_L$$

$$= V_{oc} - \frac{R_{eq} V_L}{R_L}$$

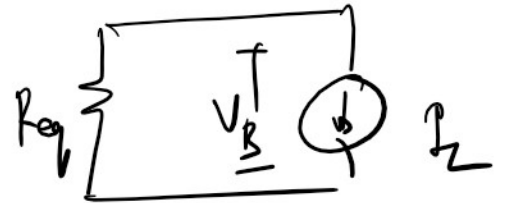

$$\Rightarrow V_L \left(1 + \frac{R_{eq}}{R_L} \right) = V_{oc}$$

$$\Rightarrow \boxed{V_L = \frac{V_{oc} R_L}{R_{eq} + R_L}}$$

