
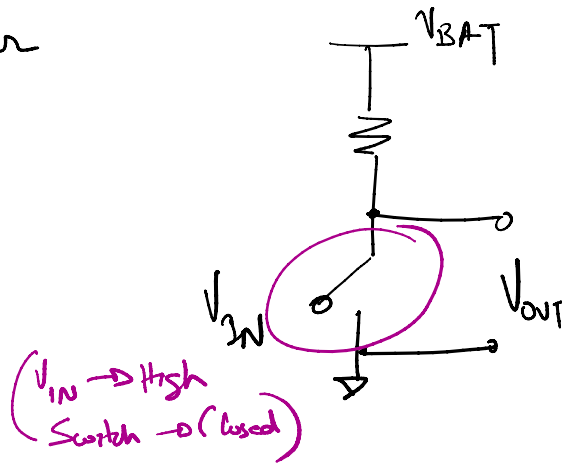



## NOT Gate / Inverter

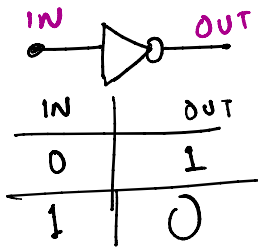


### Ideal Switch

$$R_{on} = 0$$


$$R_{off} = \infty$$

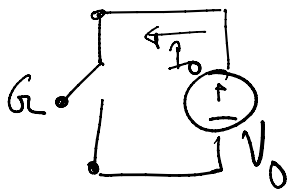


Switch on

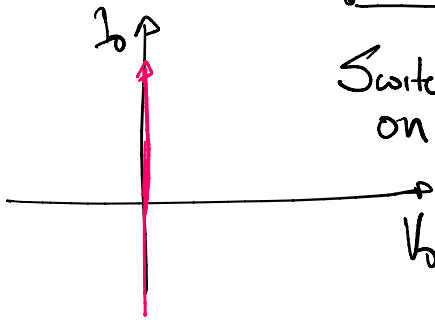


### Real Switch with $R_{on} \neq 0$

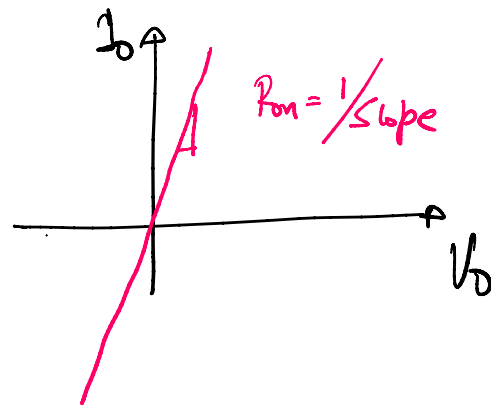


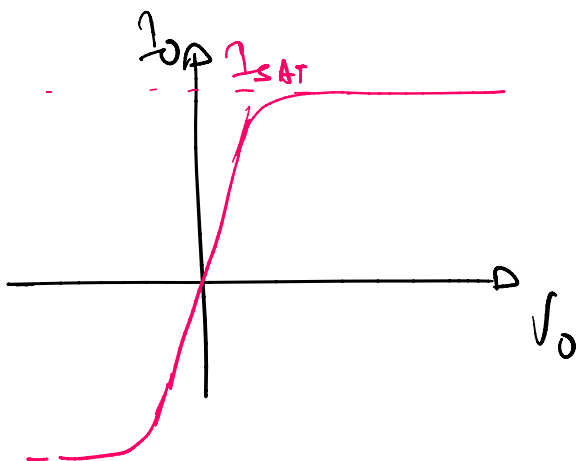Real Switch with non-zero  $R_{on}$  and current saturation:




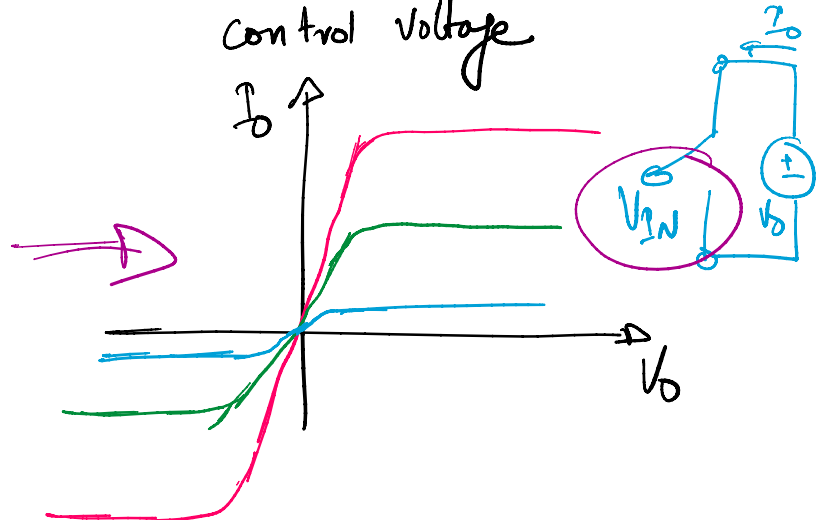Real Switch with  $R_{on}$  and  $I_{SAT}$  dependent on  $V_{IN}$  or control voltage




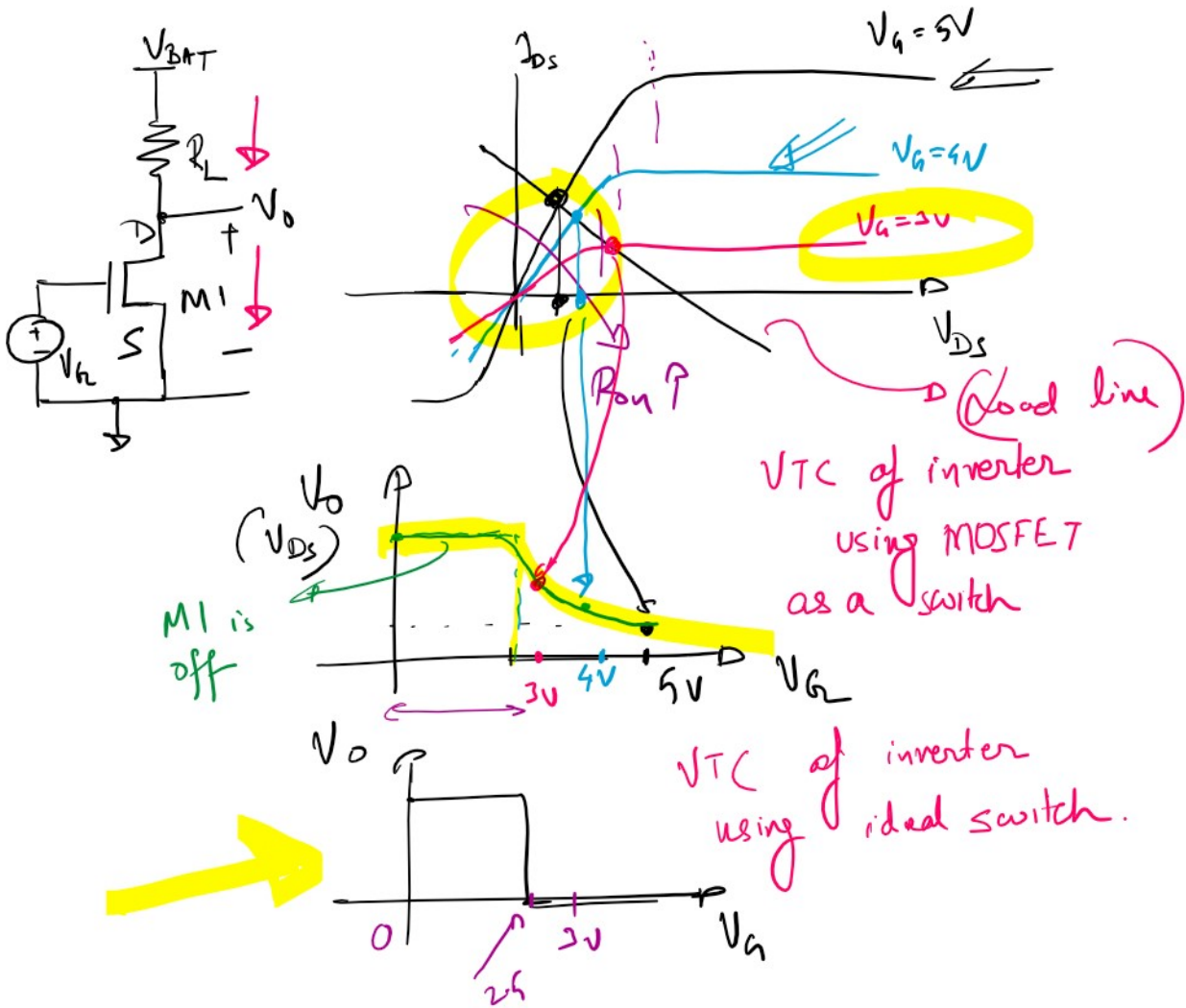


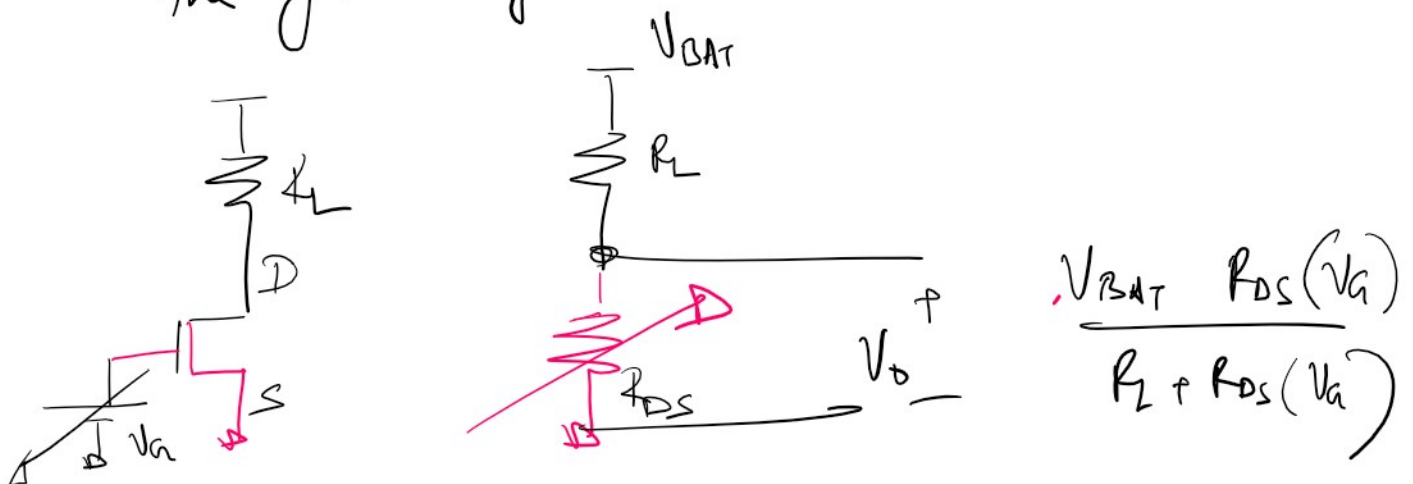A MOSFET can be thought of as a Resistor whose resistance is controlled by the gate voltage




# NOISE

# MARGIN

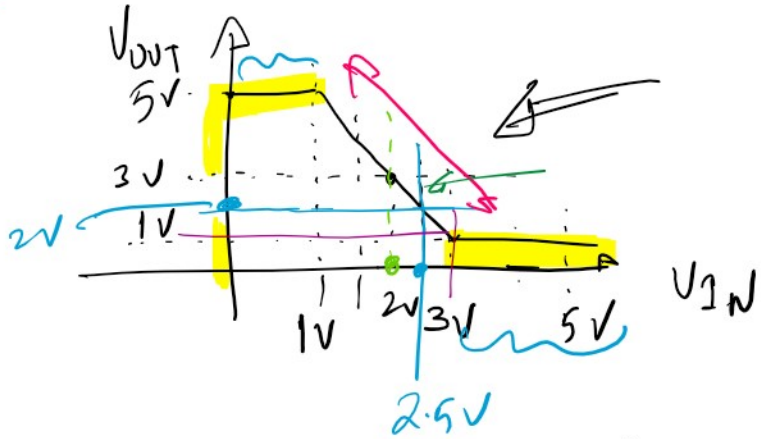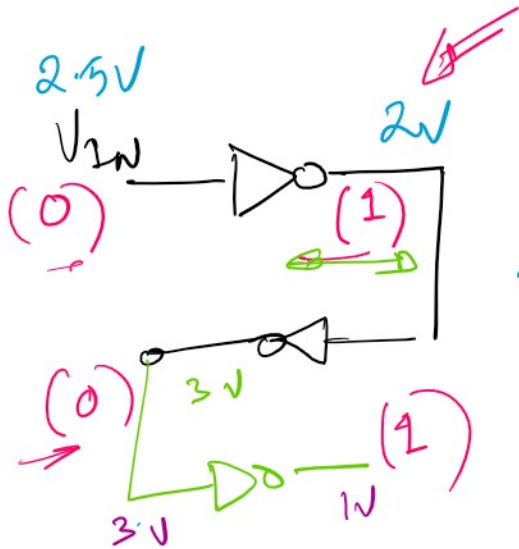

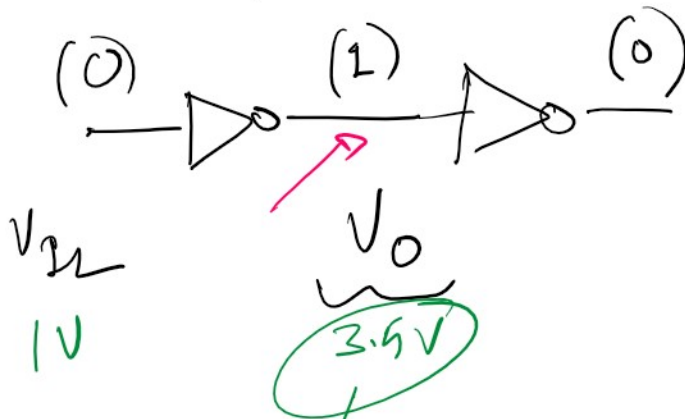Say: logic 0  $\Rightarrow$  Voltage  $< V_{IN}$   $\rightarrow$  Input  $\rightarrow$  low



Input logic 0  
valid if  $V_{IN} < 2V$   
Input logic 1  
valid if  $V_{IN} > 4V$


Not going to get recognised as valid logical i/p.

For accurate logic propagation the  $V_{OH}$  (o/p high voltage) must be




$> 0.2 < 2.2$

$V_{IH}$  (i/p high voltage level) of the next gate.

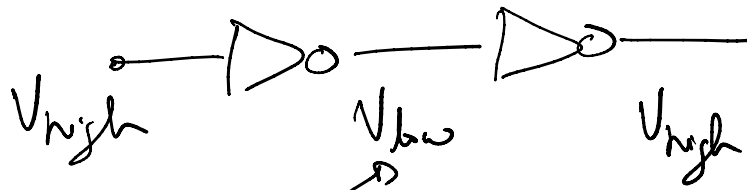$V_{2H}$  (i/p high voltage level) of the next gate.



$V_{OL}$  has to be lower than  $V_{2L}$

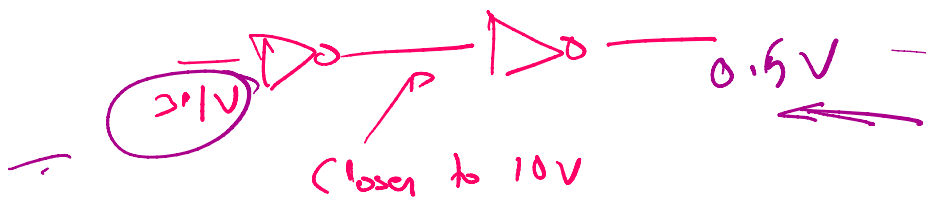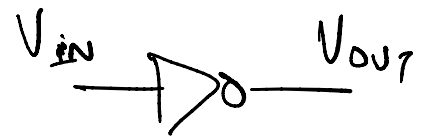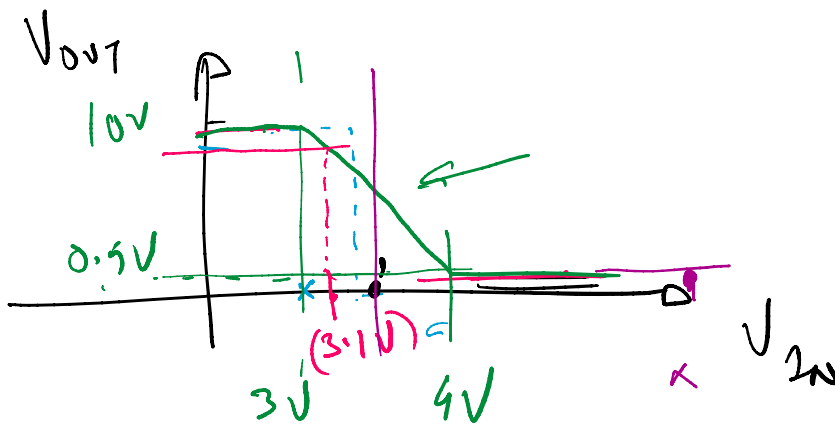

$$V_{2L} \quad V_{OH} > V_{2H}$$

$$V_{OH} - V_{2H} = NM_H$$

$$V_{2H} \quad V_{OL} < V_{2L}$$

$$V_{2L} - V_{OL} = NM_L$$

