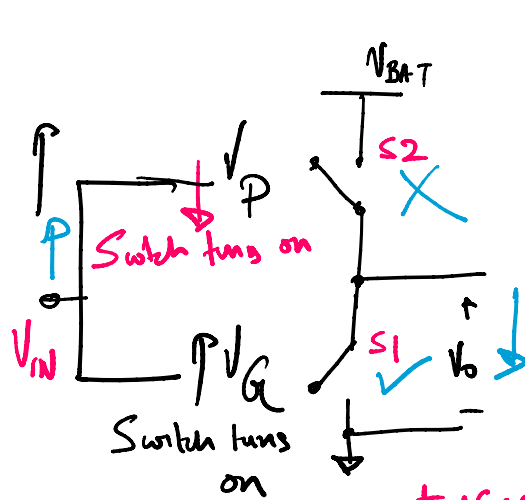


When V_G is high
Switch turns on $\rightarrow V_o \rightarrow 0$



Switch
 S_2 is of
opposite
polarity to
that of S_1

$\neq 16:2$





Assume S_1 and S_2 have ∞ off resistance.
When on, S_1 offers a resistance of $R_1 = 1k\Omega$
" " S_2 " " " " $R_2 = 1k\Omega$

Assume S_1 turns on when $V_G \geq 2V$.
" S_2 " " " $(V_{BAT} - V_P) \geq 2V$.
" $V_{BAT} = 5V$.

a) Plot the VTC for fig.2 for $0 < V_{in} < 5V$.

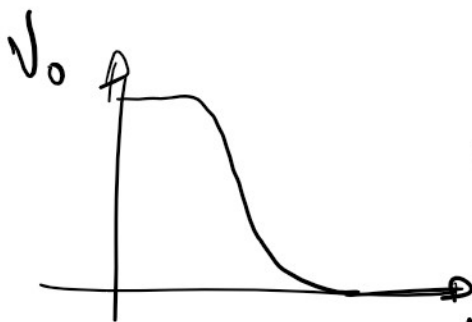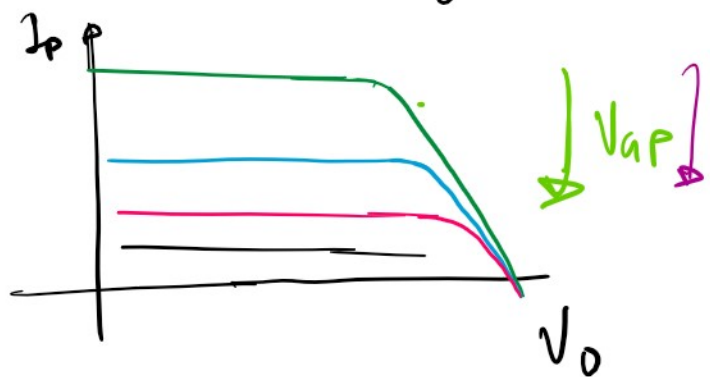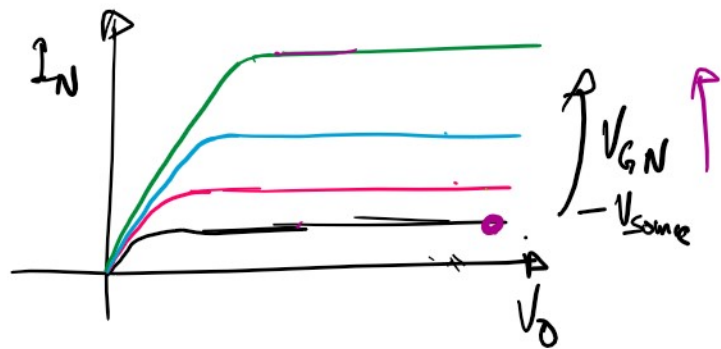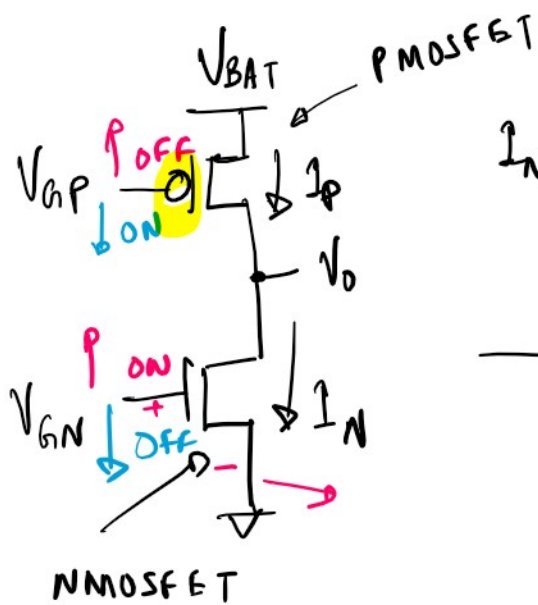b) Now assume $R_1 = 1k\Omega$ when $2V \leq V_G \leq 2.5V$
 $R_1 = 0.5k\Omega$ " $V_G > 2.5V$
 $R_2 = 1k\Omega$ " $2V \leq (V_{BAT} - V_P) < 2.5V$
 $R_2 = 0.5k\Omega$ " $(V_{BAT} - V_P) \geq 2.5V$.

Scan the following QR code to upload your answer.



VTC of a realistic inverter

$$V_{GN} = V_{GP}$$