
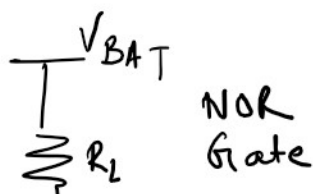
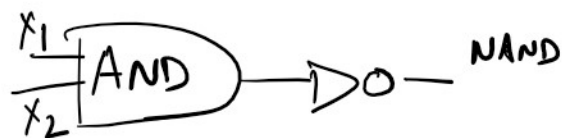
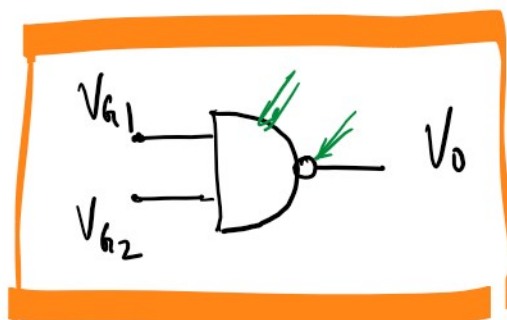
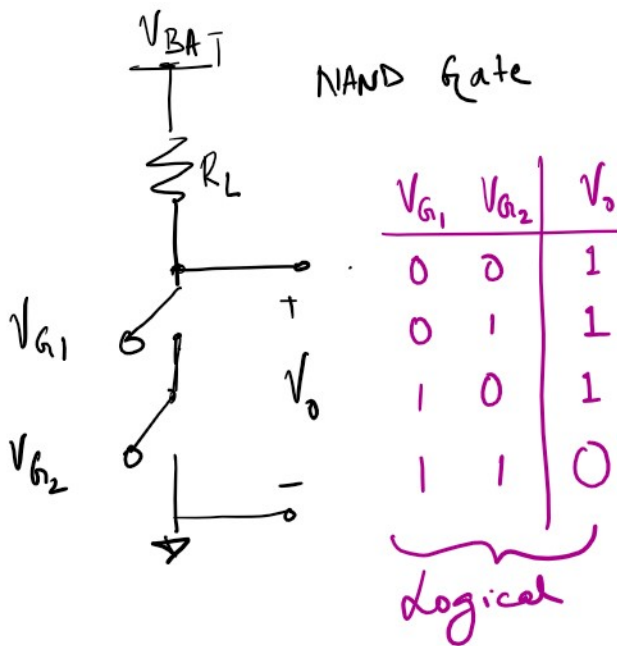



Switch activated when $V_{G1} \geq \text{Some THRESHOLD LEVEL}$


logically:

V_{G1}	V_o
0	1
1	0

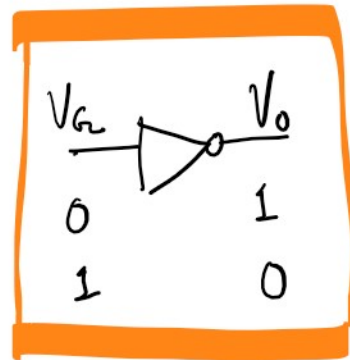



NOR Gate

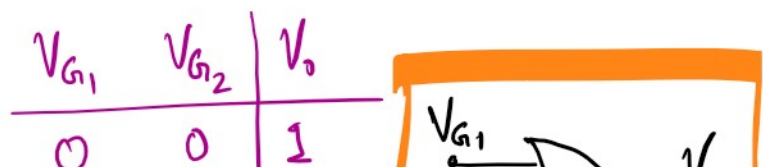


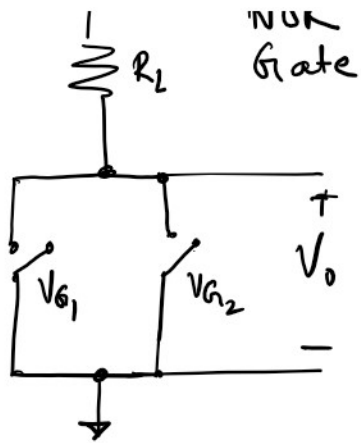


v_{i1}	v_{i2}	v_o
0	0	1
0	1	0
1	0	0
1	1	0

logical

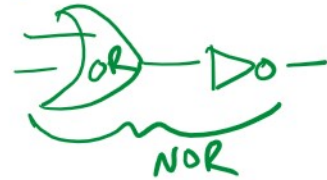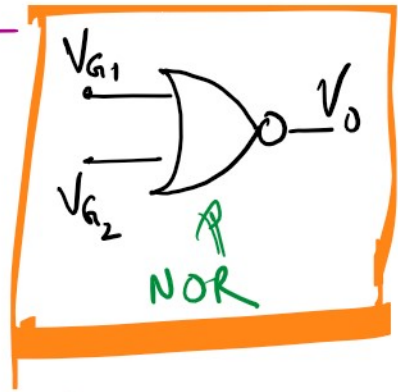


NO TIME INFORMATION!!

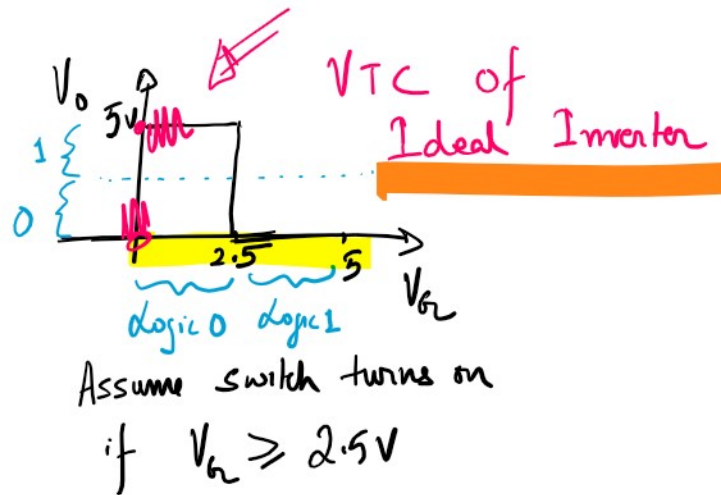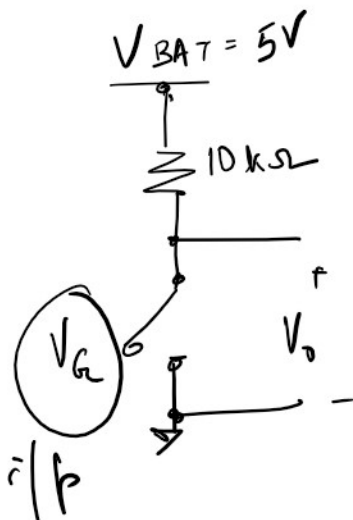


Effect of NOISE ?


Output I - V char. of a Switch

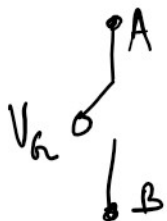

Switch off


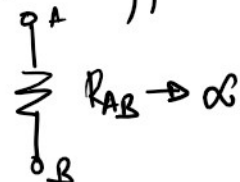


Switch on

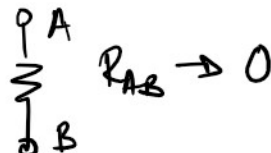

(Assume $R_{AB} = \infty$ even in practice)


(Assume some "On-Resistance")

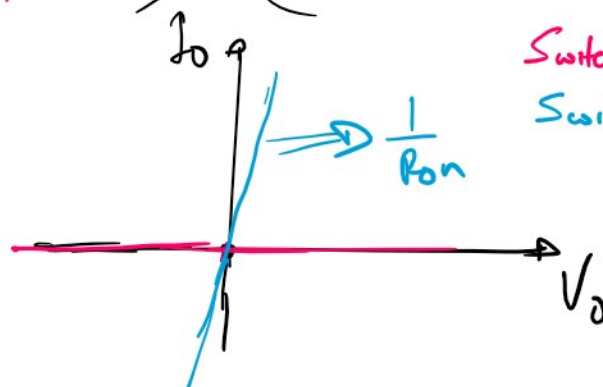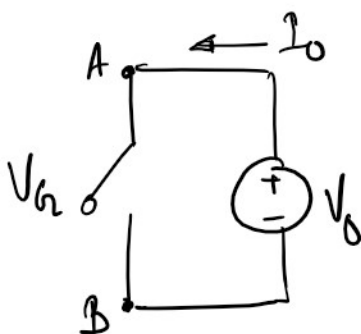


Switch is off-
Switch is on

$$R_{AB} = \infty \quad (V_G < \text{Switch on voltage})$$
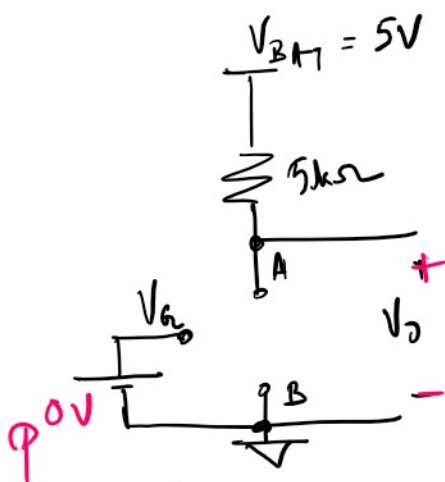
$$R_{AB} = R_{on} \quad (V_G > \text{" " " "})$$





$V_G = 0 < 2.5V$
Switch is off

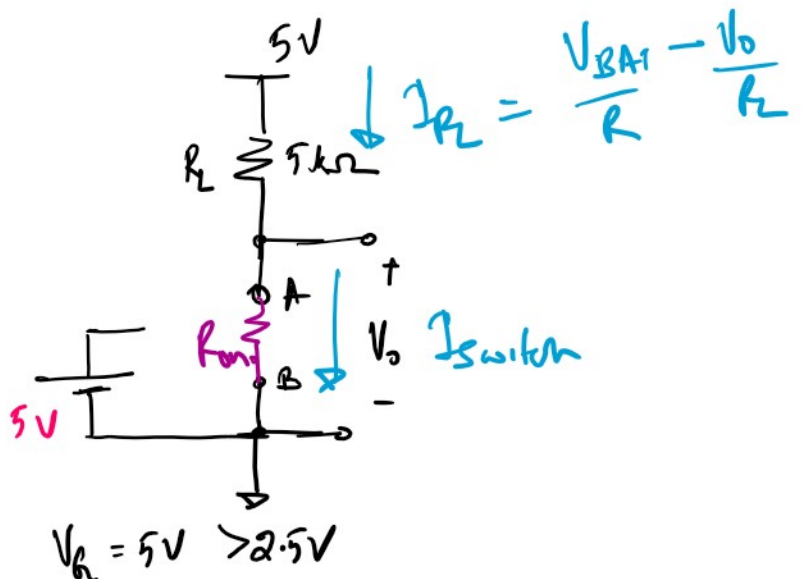

$V_G = 5V > 2.5V$

Switch is off

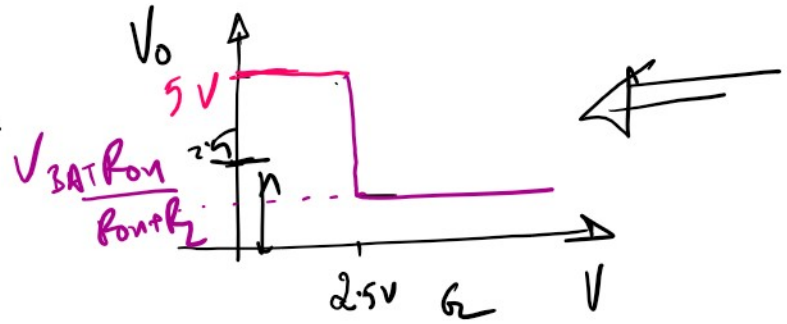
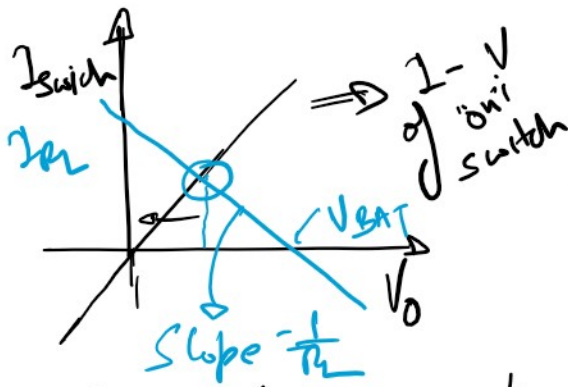


Find I_{switch} by sweeping V_o
 " I_{R_L} " " V_o

PRACTICAL


3-TERMINAL

SWITCHES

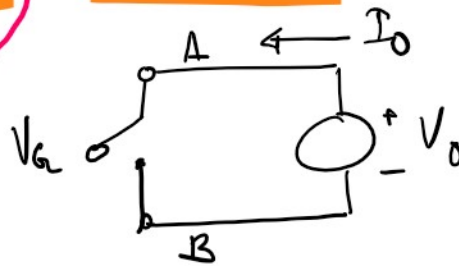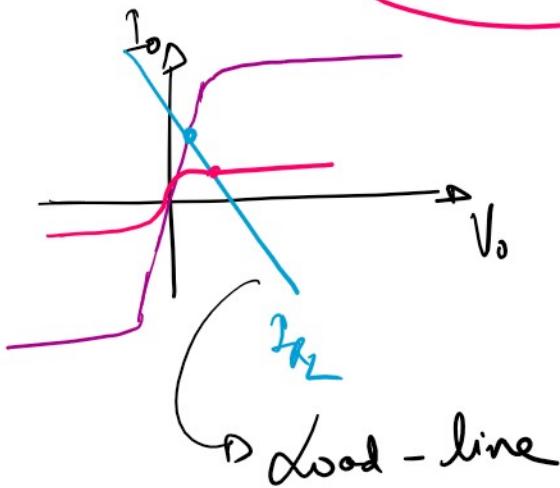

CRT / BJT / MOSFET and many more




CRT / BJT / MOSFET and many

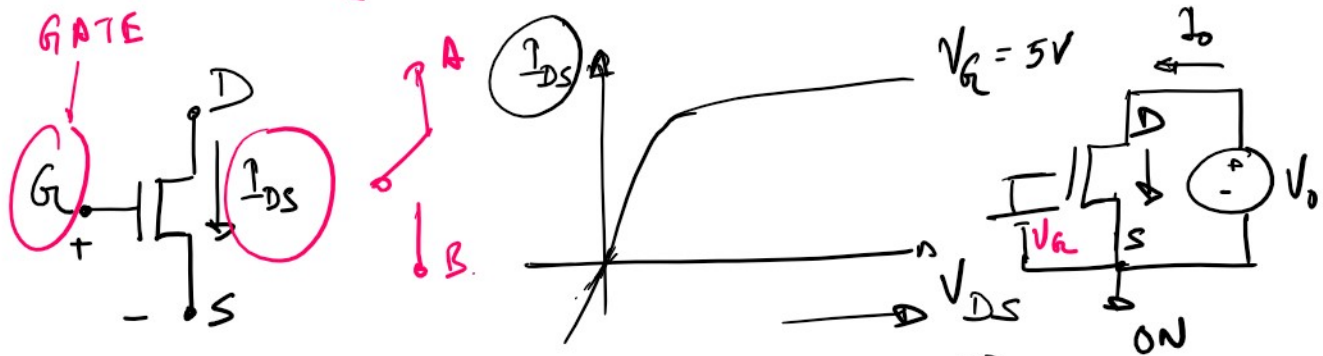


Higher voltage terminal is called DRAIN (D)
lower " " " " SOURCE (S)

MOSFET acts as a switch for a limited voltage range across it. Current saturates beyond certain o/p voltage, V_{DS} .

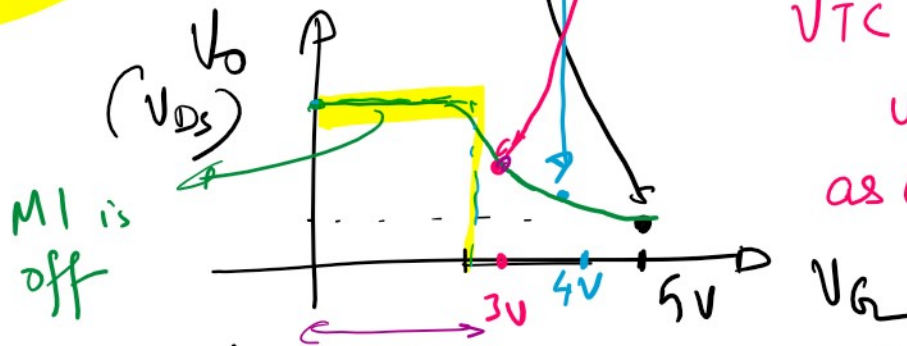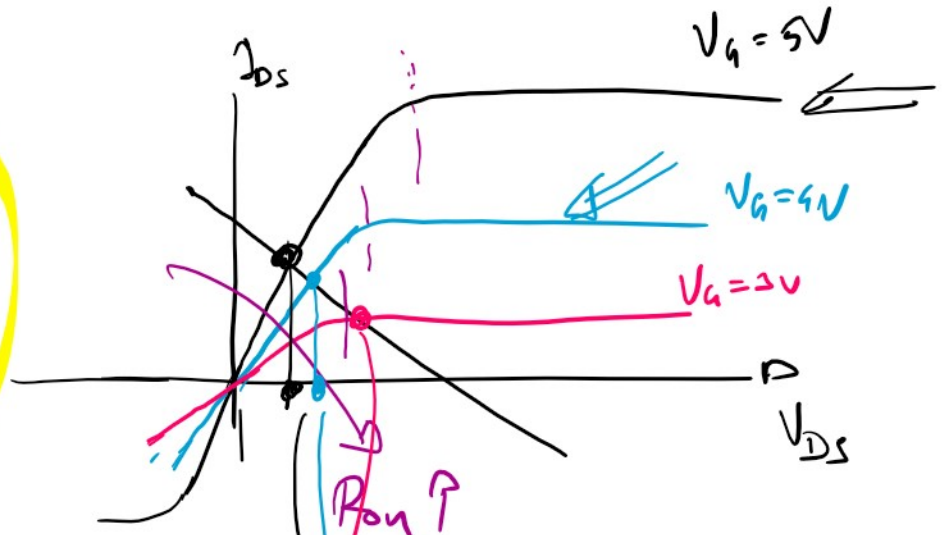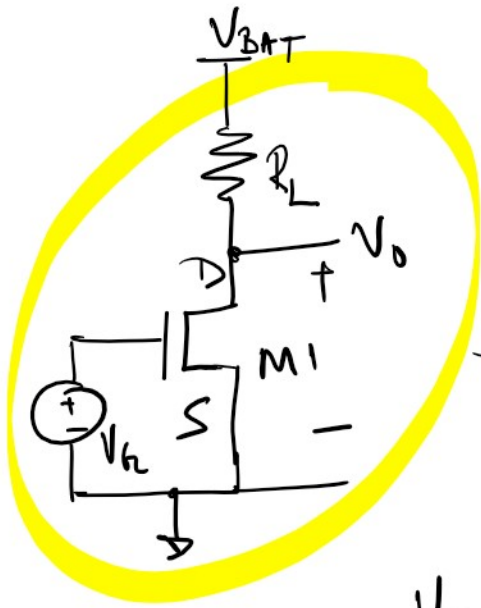The $I-V$ is also dependent on the "analog" value of the gate voltage (V_G).



VTC of inverter using MOSFET as a switch

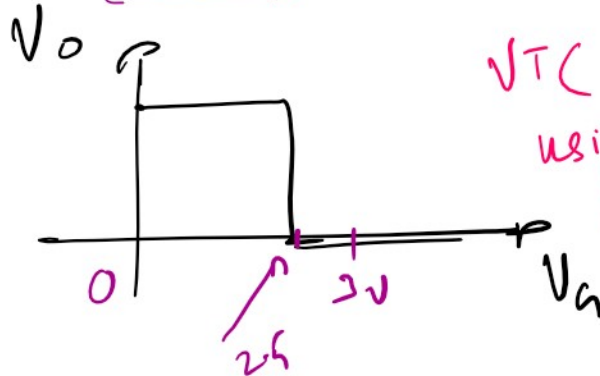

VTC of inverter using ideal switch.